

2024


APPLIED ELECTRONICS AND INSTRUMENTATION IN ENERGY HARVESTING

Full Marks: 100


Time: Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

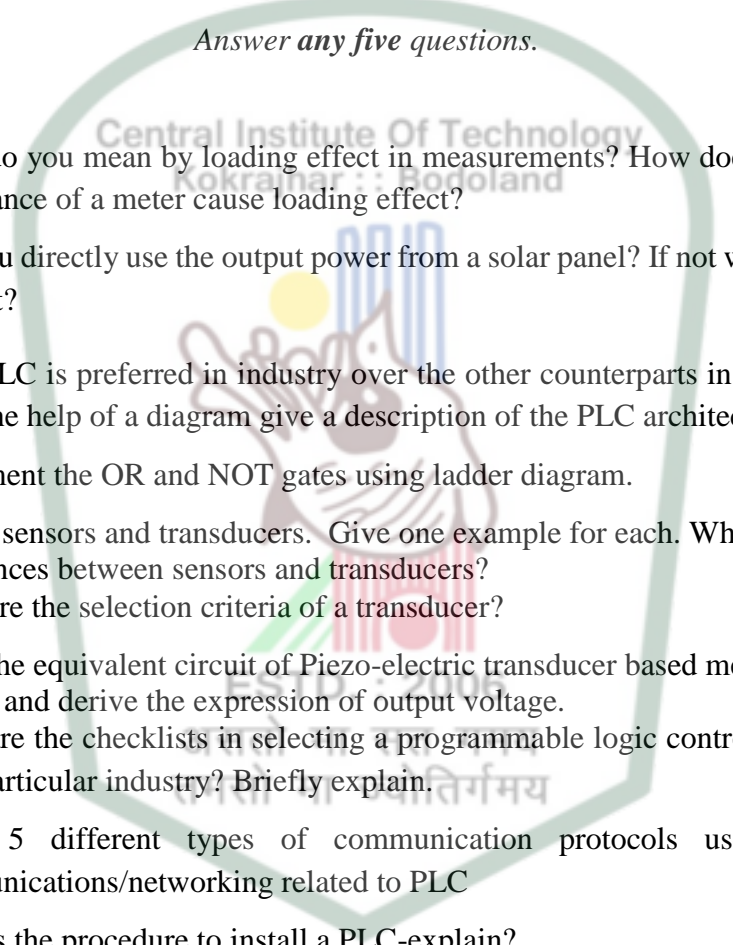- 
- 1 a) What do you mean by loading effect in measurements? How does the input admittance of a meter cause loading effect? 1+4=5
- b) Can you directly use the output power from a solar panel? If not what do you suggest? 2
- c) Why PLC is preferred in industry over the other counterparts in industries? With the help of a diagram give a description of the PLC architecture. 2+7=9
- d) Implement the OR and NOT gates using ladder diagram. 4
- 2 a) Define sensors and transducers. Give one example for each. What are the differences between sensors and transducers? 6
- b) What are the selection criteria of a transducer? 4
- c) Draw the equivalent circuit of Piezo-electric transducer based measurement system and derive the expression of output voltage. 10
- 3 a) What are the checklists in selecting a programmable logic controller (PLC) for a particular industry? Briefly explain. 8
- b) Enlist 5 different types of communication protocols used in the communications/networking related to PLC 2
- c) What is the procedure to install a PLC-explain? 5
- d) Describe a method for drawing maximum power from a solar panel. 5
- 4 Draw and explain the operation of the following: 10 + 10
- (i) Dual slope type ADC and (ii) Sample and Hold (S&H) circuit.
- 5 a) Explain Harmonic Distortion Analyser with a neat block diagram? 10
- b) What is Schmitt Trigger? Explain its operation with a circuit diagram. Also, draw its hysteresis curve. 10

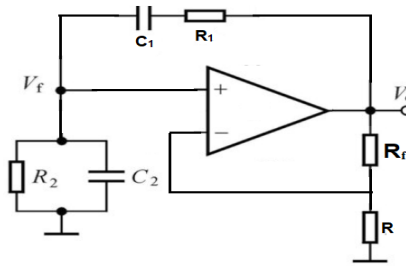- 6 a) In the Wien bridge oscillator circuit depicted in the figure below, determine the condition required for the bridge to be balanced. 10



- b) With the help of a neat block diagram explain the operation of PLL. Also explain the parameters of PLL. 10
- 7 Write Short notes on the following (any four) 5x4=20
- a) Wired Technology b) WiFi c) GSM d) Internet of Things
- e) Bluetooth f) VCO g) Sweep frequency generator

