

CENTRAL INSTITUTE OF TECHNOLOGY, KOKRAJHAR

(Deemed to be University)

KOKRAJHAR :: B.T.A.D. :: ASSAM :: 783370

END – SEMESTER EXAMINATION

PG

Session: Jan-June, 2025

Semester: 2nd

Time: 3Hrs.

Full Marks: 100

Course Code: MGE213

Course Title: Advanced Power Electronics

ANSWER ANY FIVE QUESTIONS:

1. a. What is equalization circuits. Derive the expression for equalization resistance of a series equalization circuit. 10
b. A resistive load of 10Ω is connected through a half wave SCR circuit through 220, 50Hz single phase source. Calculate the power delivered to the load for firing angle of 60° . Also find the input power factor. 6
c. A dc battery is charged through a resistor R as shown in fig.1. Derive an expression for the average value of charging current in terms of V_m , E, R etc. on the assumption that the SCR is fired continuously. For an AC source voltage of 230V, 50Hz find the value of average charging current for $R=8\Omega$ and $E=150V$. 4

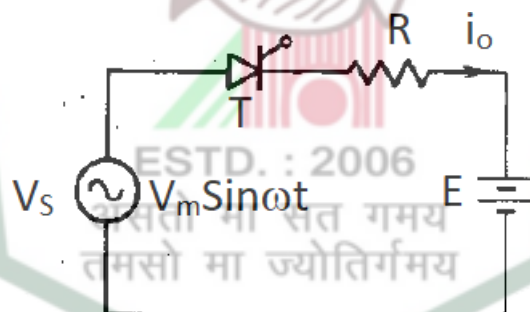


Fig. 1

2. a. What is UPS? Explain the working of short and no break UPS. 10
b. What is a chopper? Derive the input output relation of buck and boost chopper. 10
3. a. A step up chopper has an input voltage of 150V. The voltage output needed is 450V. Given, that the thyristor has a conducting time of 150μseconds. Calculate the chopping frequency. 6
b. A separately excited DC motor is supplied from a 230V, 50 Hz source through a single phase half wave controlled converter. Its field is fed through a 1-phase semi converter with zero degree firing angle delay. Motor resistance $r_a=0.7\Omega$ and motor

constant is 0.5 V-sec/rad. For rated load torque of 15nm at 1000rpm and for continuous ripple free currents, determine-

- i. firing angle delay of the armature converter
 - ii. rms values of thyristor and freewheeling diode currents
 - iii. input power factor of the armature converter 14
4. a. For a type A chopper dc source voltage is 230V, load resistance is 10Ω . Voltage drop across the chopper is 2V when it is on. For a duty cycle of 0.4 calculate - 8
 - i. average and rms values of output voltage
 - ii. chopper efficiency
- b. A single phase half bridge inverter has a resistance of 2.5Ω and input DC voltage of 50V. Calculate the following - 12
 - i. The RMS voltage occurring at the fundamental frequency
 - ii. The power output
 - iii. Peak current and average current
 - iv. Harmonic RMS voltage
 - v. Total harmonic distortion
5. a. What is SMPS? Explain the working of any one configuration of SMPS. 10
 - b. What is resonant converter? Explain load resonant converter. 10
6. Write short notes on- 10x2=20
 - a. Sepic converter
 - b. Multilevel inverter