

2021

ELECTRICAL CIRCUITS AND NETWORKS

Full Marks: 100

Time: Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

1. a) Determine the equivalent resistance between terminals A and B in figure 1. 6

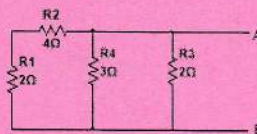


Figure 1

- b) State Kirchhoff's Voltage Law (KVL) and find the current in figure 2 using KVL. 7


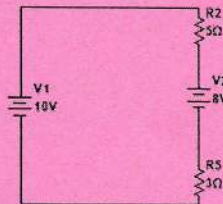


Figure 2

- c) State Kirchhoff's Current Law and explain using a suitable circuit diagram. 7
2. a) Find the voltage across resistor R1 in figure 3 using voltage divide rule. 5

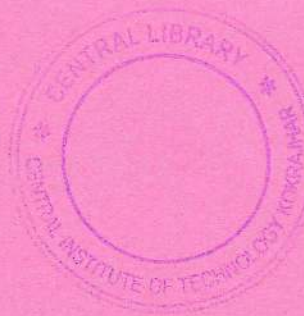

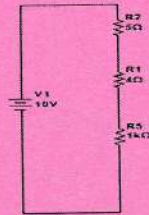


Figure 3

- b) What is current divide rule? Explain with a circuit diagram. 7
- c) State Norton's Theorem. Show the application of Norton's Theorem in a circuit. 8

3. a) Find the currents I_1, I_2 and I_3 in figure 4 using mesh analysis. 10

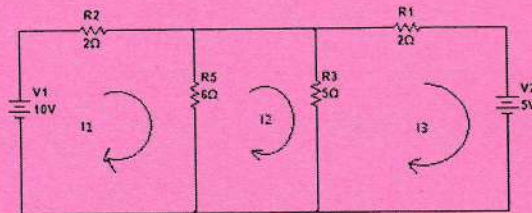


Figure 4

- b) Find currents I_1 and I_2 in figure 5 using nodal analysis. 10

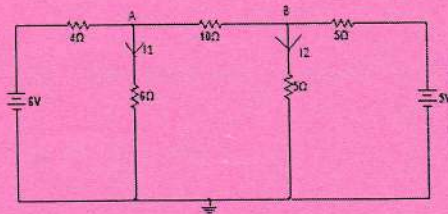


Figure 5

4. a) Determine the current I in figure 6 using Thevenin's Theorem

10

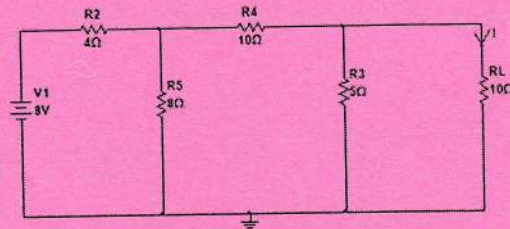


Figure 6

- b) Determine current I through 2Ω resistor in figure 7 using Superposition Theorem.

10

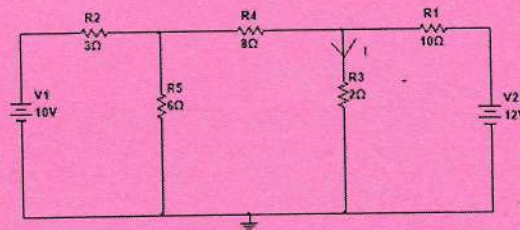


Figure 7

5. a) Draw the phasor diagram for the following cases:

10

- i. A.C. Through pure ohmic resistance alone.
- ii. A.C. Through pure inductance alone.
- iii. A.C. Through pure capacitor alone.
- iv. A.C. through series resistor and inductor circuit.
- v. A.C. through series resistor and capacitor circuit.

- b) A 50 Hz sinusoidal waveform of voltage $v(t)=100\sin 314t$ is applied to a series R-L circuit. The values of resistance and inductance are 5Ω and 0.4mH respectively. Determine the following

7



- i. RMS Value of the voltage waveform
 - ii. Inductive reactance X_L .
 - iii. Impedance Z_L
 - iv. RMS Value of current.
 - v. Phase angle
 - vi. Power factor.
- c) What is maximum power transfer theorem? 3
- 6 a) The instantaneous value of a waveform is given as $v(t)=10\sin 314t$. What is the maximum value, frequency and time period of the waveform? 4
- b) What is the function of resistor, capacitor and inductor in a circuit? 6
- c) Define the following 10
- i. R.M.S value of an alternating waveform.
 - ii. Average value of an alternating waveform.
 - iii. Phase difference between two alternating waveforms.
 - iv. Impedance.
 - v. Reactance.
- 7 Write short notes on the following: 20
- i. Star/Delta Transformation.
 - ii. Source conversion.
 - iii. R.M.S value and Average value of an alternating waveform
 - iv. Independent and dependent sources.
 - v. Active, passive and apparent power.

