

Total No. of printed pages = 6

19/3rd Sem/UECE304

2021

NETWORK THEORY


Full Marks – 100

Time – Three hours

The figures in the margin indicate full marks for the questions.

Answer any *five* questions.

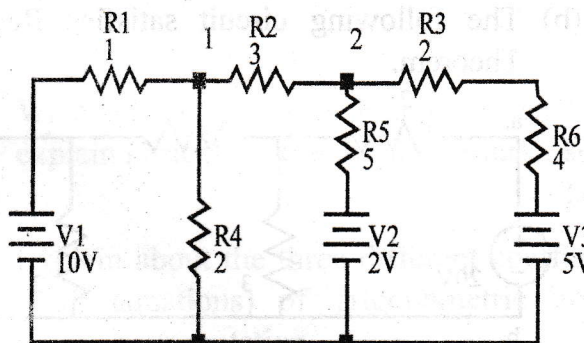
- (a) Point out the main differences between Nodal and Mesh analysis. 5
- (b) Find the voltage (V) at node 1 in the circuit shown below by using Nodal analysis. 8




[Turn over



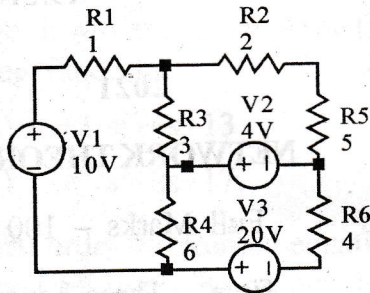
(c) Find the current I_3 (A) from the figure given below by using Mesh analysis. 7



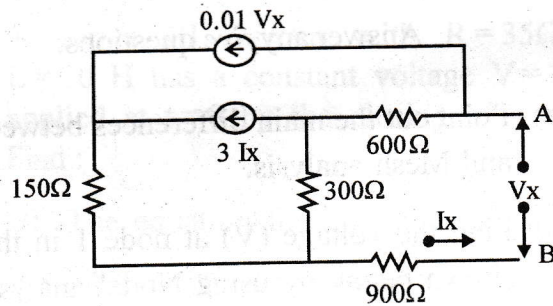2. (a) In the provided circuit below, find the value of open circuit voltage and the Thevenin resistance between terminals a and b. 5




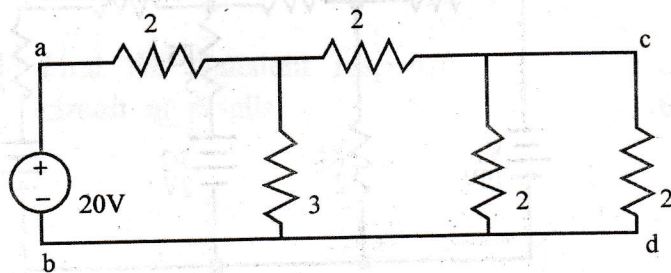(b) The following circuit satisfies Reciprocity Theorem.




Write true or false. 1

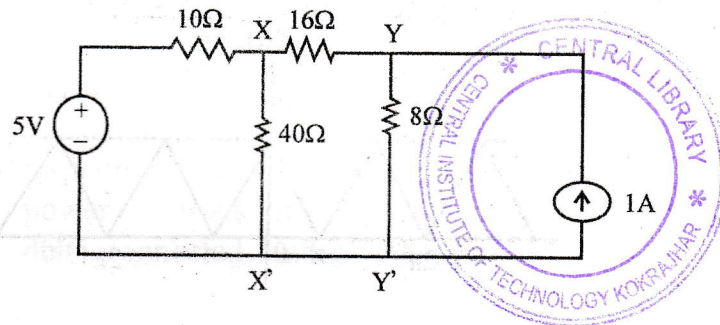- (c) The circuit which satisfies Reciprocity Theorem is called ? 1
- (a) Short circuit (b) Open circuit
(c) Linear circuit (d) Non-linear circuit
- (d) Define maximum power transfer theorem. Also find the condition of maximum power transfer in an electrical circuit. 1+6=7
- (e) A circuit is given in the figure below. Find the Norton equivalent as viewed from terminals x and x'. 6




3. (a) What do you mean by Fourier series ? Also explain Dirichlet's condition of Fourier series. 2+4=6
- (b) Explain about the three different coefficients (with equations) of Trigonometric Fourier series representation. 6

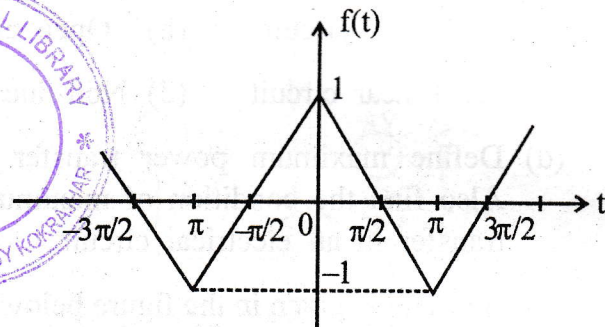- (c) Obtain the trigonometric Fourier series Representation for the signal shown below :




8

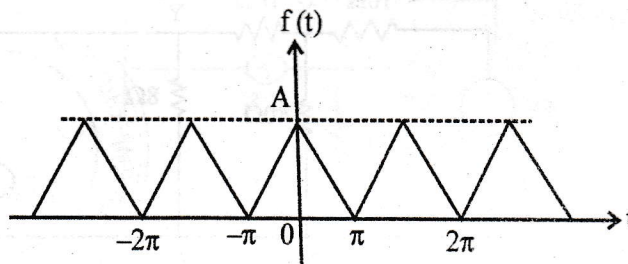4. (a) Find the exponential Fourier series of the Waveform as shown in the following figure. 8




- (b) A series RL circuit with $R=10 \Omega$ and $L=5H$ contains a current $i(t) = 10 \sin 1000 t + 5 \sin 3000 t + 3 \sin 5000 t$. Find the effective value of voltage. 7
- (c) Differentiate between the Average value and RMS value of periodic wave in Fourier series representation by using proper equations. 5

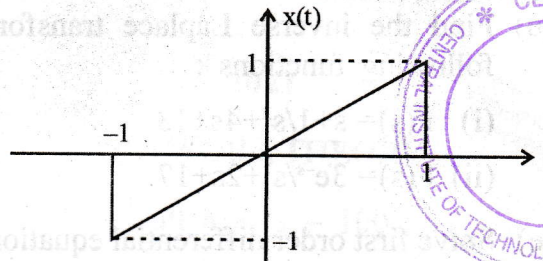5. (a) Find the Fourier transform of the time signal as shown in figure below. 7



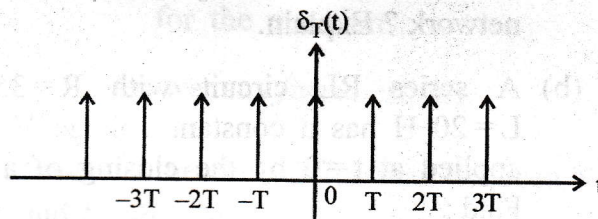- (b) Find the Fourier transform of an impulse train shown in the figure below: 6



- (c) Explain the differences between voltage and power relations of star-connected load and delta connected load of three phase circuits. 4
- (d) Differentiate between Balanced and Un-balanced three phase circuits. 3
6. (a) Find the Laplace transform of $x(t) = \sin^2 \omega_0 t u(t)$ 3
- (b) Find the Laplace transform of $x(t) = te^{-3t} u(t)$. 2

- (c) Find the convolution of $h(t) = e^{-3t}$ and $f(t) = e^{-7/8t}$. 2
- (d) Find the inverse Laplace transform of the following functions :
- (i) $F(s) = s+1/s^2+4s+13$
- (ii) $F(s) = 3e^{-s}/s^2+2s+17$. 3+3=6
- (e) Solve first order differential equation of series RC circuit by using its proper diagram. 7
7. (a) What is known as Z-parameter of two port network ? Explain. 7
- (b) A series RL circuit with $R = 35\Omega$ and $L = 20\text{ H}$ has a constant voltage $V = 100\text{ V}$ applied at $t = 0$ by the closing of a switch. Find :
- (i) The equation for i .
- (ii) The current at $t = 1.65\text{ s}$.
- (iii) The expressions for V_R and V_L .
- (iv) The time at which $V_R = V_L$. 7
- (c) Find the transient response of series RL circuit in details. 6

