

Total number of printed pages: 2

Programme: UG/3rd/UECE302

JUNE 2024

DIGITAL SYSTEM DESIGN

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

1. a) How can we represent negative numbers in binary form? Compare different methods by representing $(-61)_{10}$ in an 8-bit binary format. 5
- b) State all the basic postulates of Boolean algebra. 5
- c) Design a 4-bit carry look-ahead binary adder. Discuss its advantage over a ripple carry adder. 10
2. a) What is the advantage of using BCD codes? Explain how we can implement BCD addition using binary adders. 6
- b) Design a gray to binary code converter circuit using K-map method. 6
- c) Express the Boolean function $F(w, x, y, z) = \sum m(3,4,5,7,10,11)$ in SOP form. Implement the same using only 2x1 multiplexers. 8
3. a) Design a single bit comparator. Using three such comparators, design a 3-bit comparator circuit. 8
- b) Design an 8x3 priority encoder with a 'valid' output. Find the simplified Boolean expression for each output. 6
- c) Design an array multiplier which can multiply any two 3-bit numbers. 6
4. a) Show the design procedure to construct a J-K flip-flop from a T flip-flop. 6
- b) Explain in detail (with necessary circuit diagram) two ways in which we can construct an edge-triggered J-K flip-flop. 8
- c) With the help of circuit diagram, discuss the difference between a mod-5 ripple counter and a synchronous counter. 6
5. a) Draw the diagram of 4-bit Johnson counter and enumerate all its states. 5
- b) Design a sequence detector using D flip-flops which can detect a 4-bit sequence '0110' with overlap. 10

- c) Design a frequency divider which can divide the frequency of an input square wave by a factor of 40. 5
- 6. a) What are PLDs? Using an example, compare the advantages and disadvantages of PLA and PAL. 8
- b) With the help of a neat circuit diagram, explain the transfer characteristics of a TTL Inverter. Discuss the function of each transistor in the circuit. 8
- c) Draw the circuit diagram to realize a CMOS 2-input OR gate and verify its truth table. 4

.....