

2022



NETWORK THEORY

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

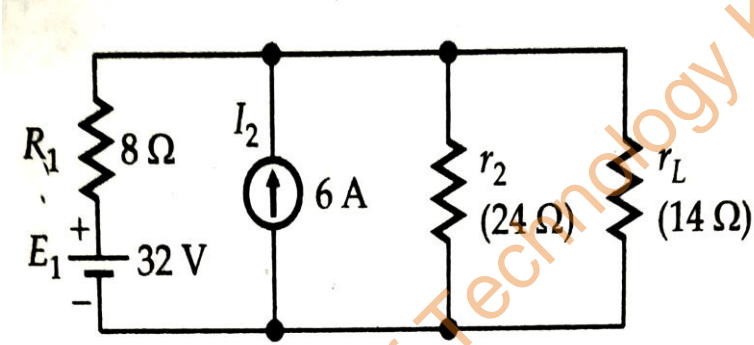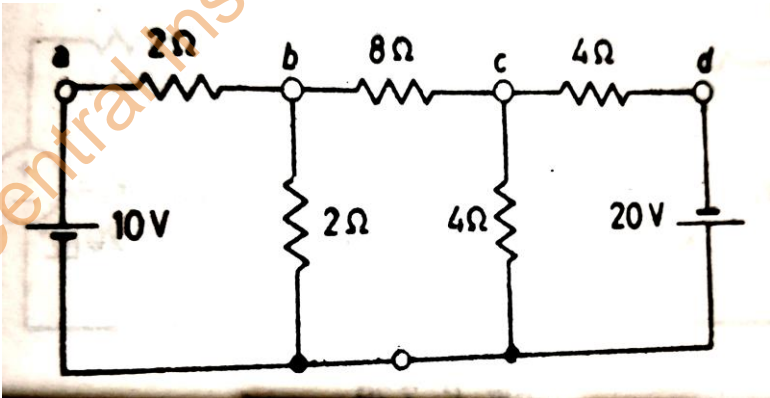1.	a)	<p>What is meant by short and open circuits? Differentiate a network and circuit. In the circuit shown in figure 1(a), find the current through r_L.</p>  <p style="text-align: center;">Figure 1(a)</p>	3+4+6=13
	b)	<p>Determine the current passing through the different branches of the circuit in figure 1(b), by the principle of superposition.</p>  <p style="text-align: center;">Figure 1(b)</p>	7
2.	a)	<p>Define linear and non-linear network. What are the applications of Maximum power transfer theorem?</p>	4+3=7
	b)	<p>State and prove superposition theorem. Draw the Thevenin's equivalent of</p>	6+7=13

the circuit shown in figure 2(b) and find the load current.

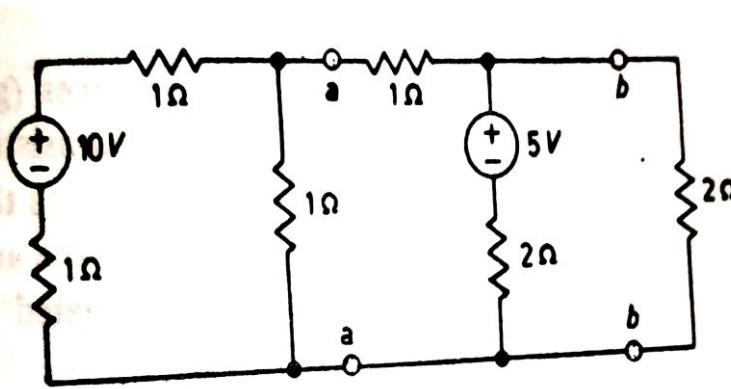


Figure 2(b)

3 a) Express the Fourier series coefficients (i) for trigonometric function, (ii) for complex exponential. Find the Fourier series coefficients of the waveform shown in figure 3(a).

5+5=10

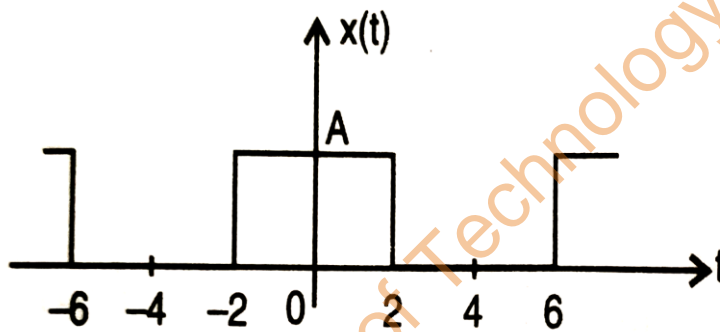


Figure 3(a)

b) Define Fourier transform of a continuous-time function. Find the Fourier series representation of waveform given in figure 3(b) (using trigonometric Fourier series). 4+6=10

4+6=10

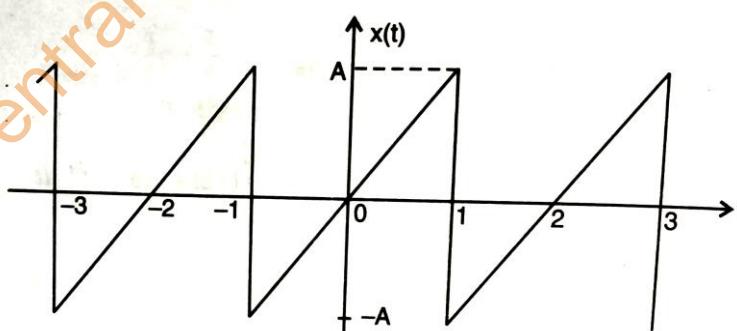
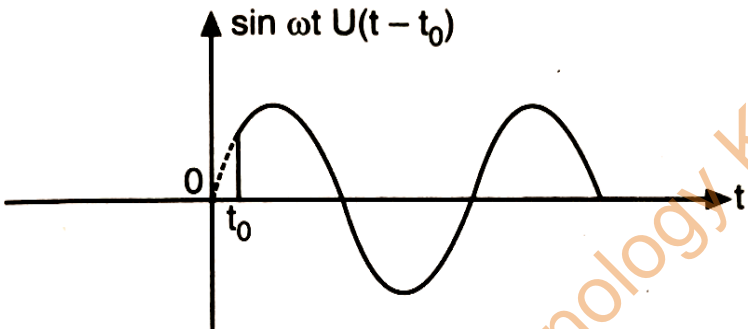
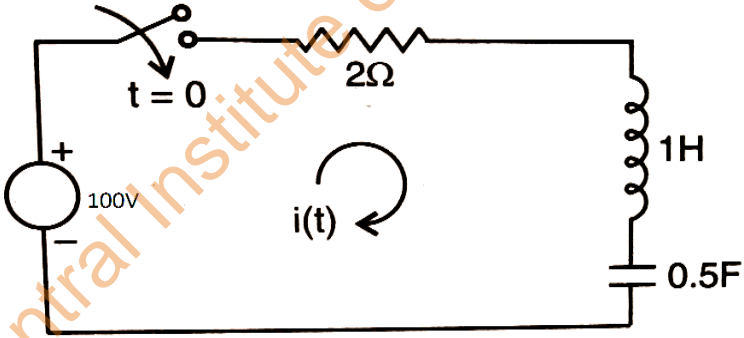


Figure 3(b)

4. a) Use Laplace transform method to solve the differential equation

6

		$\frac{d^2v}{dt^2} + \frac{3dv}{dt} + 2v = 4U(t)$ [Given $v(0^-) = 0$ and $\frac{dv}{dt}(0^-) = 5$]	
	b)	Define Laplace transform and inverse Laplace transform. Find the inverse Laplace transform of the following function (i) $F(s) = \frac{s+5}{s(s^2+2s+5)}$ (ii) $I(s) = \frac{1}{s(s+1)^2(s+2)}$	5+4+5=14
5	a)	Find the Laplace transforms of the following functions. (i) $e^{-at}U(t)$ (ii) $e^{-at}U(t-b)$ (iii) $e^{-a(t-b)}U(t-b)$ (iv) Laplace transform of the following sinusoidal function.	2+3+3+5=13
		 <p>The graph shows a sinusoidal wave starting at time t_0 on the horizontal axis. The vertical axis is labeled $\sin \omega t U(t - t_0)$. The wave starts at the origin $(0,0)$ and begins its oscillation at $t = t_0$.</p>	
	b)	In the series R-L-C circuit shown in figure 5(b), there is no initial charge on the capacitor. If the switch S is closed at $t=0$, determine the resulting current.	7
		 <p>The circuit diagram shows a series R-L-C circuit. It consists of a 100V DC voltage source, a switch labeled 't = 0', a 2Ω resistor, a 1H inductor, and a 0.5F capacitor. The current $i(t)$ is indicated by a circular arrow in the center of the loop.</p>	
		Figure 5(b)	
6	a)	What is the concept of complex frequency? Check whether given functions are suitable in representing the transfer functions or not? (i) $G_{21}(s) = \frac{5s+2}{5s^3+4s^2+1}$ (ii) $G_{21}(s) = \frac{2s^2+5}{3s^2+9s+1}$ (iii) $\alpha_{21}(s) = \frac{2s^2+5s+1}{s+7}$ (iv) $\frac{1}{s^2+2s}$	4+1.5×4=10
	b)	Explain the concept of poles and zeros in a network function. Find the driving point impedance of the network shown in figure 6(b). Find the	3+3+4=10

poles and zeros of the network and locate them in the s-plane.

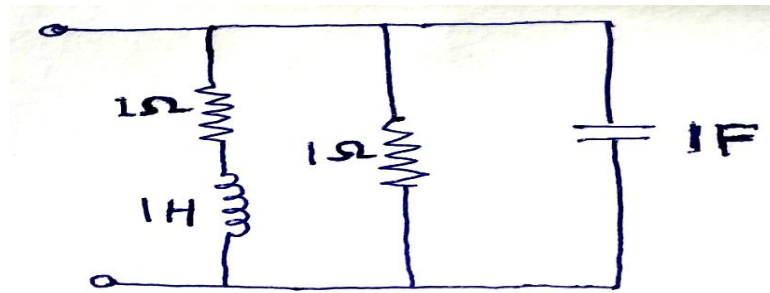


Figure 6(b)

7

a) Define all the characteristics of filter networks. Prove that the characteristics impedance of symmetrical T- network $Z_{OT} = \sqrt{Z_{OC}Z_{SC}}$, where Z_{OC} is open circuit impedance and Z_{SC} is short-circuit impedance.

4+5=9

b) Find the short circuit and open circuit impedances of the network shown in figure 7(b).

6

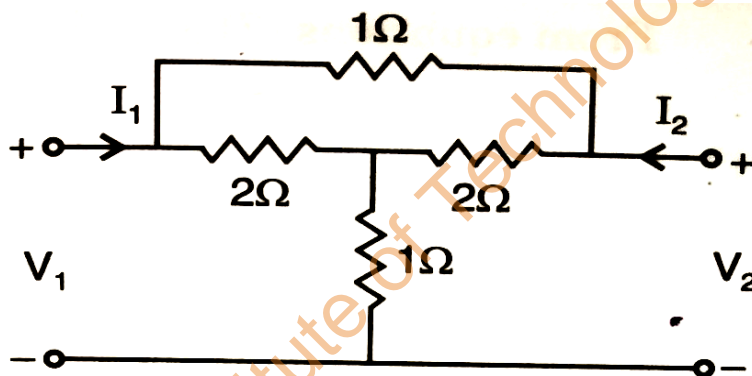


Figure 7(b)

c) Determine the ABCD parameters of the two networks connected in cascade as shown in figure 7(c).

5

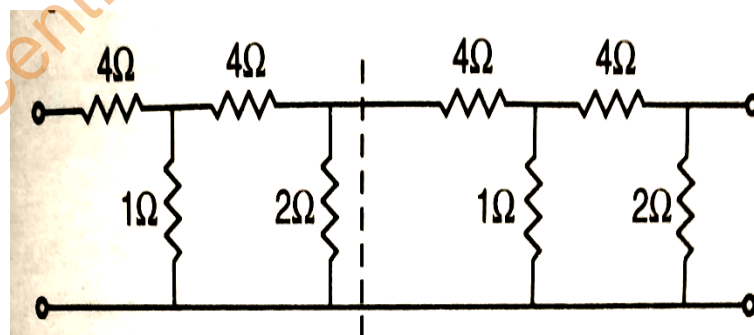


Figure 7(c)