

Total number of printed pages:2

UG/3rd/UECE306

2024

SUBJECT NAME : Digital Electronics & Logic Design

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

- Q.1 a) Prove that $x+yz=(x+y)(x+z)$ 5
- b) Use basic gate (without simplifying the function) to realize $Y=abc'+a'b'c'+ab'c$ 5
- c) Use only NOR gate to realize $Y=(a+b')(a'+c)$ 4
- d) Use Boolean algebraic techniques to simplify $f(x,y,z)=xyz+xyz+(x'+y'+z')+xy'z'$ 3
- e) Convert
- i) hexadecimal FA1 into binary ii) 0011111 into octal iii) decimal 45 into octal 3
- Q.2 Use k-map method to simplify the following 4+5+6+5=20
- a) $f(x,y,z)=\sum m(0,1,2,3)$
- b) $f(w,x,y,z)=\sum m(0,1,2,3,7,9,10)$
- c) $f(w,x,y,z)=\sum m(0,2,7,9,10,11,12)+d(1,3,15)$
- d) $f(w,x,y,z)=\pi M(0,1,3,9,10)$
- Q.3 Design following combinational circuits 5+7+5+3=20
- a) 4:1 multiplexer.
- b) Full subtractor
- c) 4:2 Encoder

d) Half adder

Q.4 Describe following circuits operation with circuit diagram , truth table etc. 5X4=20

a) S-R latch b) J-K latch c) Master slave flip flop d) Pulse triggered flip flop.

Q.5 Describe 2 bit asynchronous counter operation with block diagram , timing diagram, counting status table etc. 20

Q.6 a) State and prove de-morgan's theorem 2+6=8

b) Design a 1:8 De-Multiplexer . 6

c) Differentiate the following 3X2=6

i) Combinational & sequential circuit ii) Edge & pulse triggering

Q.7 a) Describe 4 bit right shift register operation with block diagram , timing diagram etc. 14

b) Use Boolean algebraic techniques to simplify 3+3=6

i) $(a+b+c)(a+b+c')(a+b')+abc$ ii) $x.x+x.x'+(1+x)'+(xy)'$