

Total number of printed pages: 2

UG/3rd/UECE306

2024

SUBJECT NAME: Digital Electronics & Logic Design

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

1.	a)	Use x-or gate to realize $a \oplus b \oplus c$.	1
	b)	Use nand gate to realize $a+b$.	1
	c)	Use basic gates to realize $a+b(cd')$.	1
	d)	Write down the truth table and symbol of a positive edge triggered D master slave flip flop.	2 +1=3
	e)	Design a 4:1 multiplexer.	6
	f)	Explain the function of a 2 bit asynchronous counter with circuit diagram, timing waveform etc	8
2.	a)	Draw the circuit of S_R latch and explain the truth table	2+2=4
	b)	Write down the truth table of a 2 bit binary to gray converter	1
	c)	Design a 1:4 de-multiplexer	5
	d)	Draw the circuit of a j-k latch	2
	e)	Convert a s-r latch into j-k latch using synthesis method	7
3.	a)	Simplify $xy + cv + (cv)'yx + (xy)' + 1$.	1
	b)	Use nor gate to realize ab .	1
	c)	Use k-map to simplify $\sum m(0,4,5,9,7,14) + d(1,6,13)$.	5
	d)	Draw the circuit diagram of a 4 bit gray to binary converter	3
	e)	Design a Mod-3 counter using j-k master slave flip flop	10
4.	a)	Draw and explain the state transition table of j-k flip flop	2+2=4
	b)	Plot Q output for a positive edge triggered j-k master slave flip flop for	2

		single clock pulse when $j=0$ and $k=0$	
	c)	Plot Q output for a negative edge triggered s-r master slave flip flop for two clock pulse (1 st clk pulse $s=1$ and $k=0$ 2 nd clk pulse $s=0$ $r=0$)	2
	d)	Design a Mod-5 counter using j-k master slave flip flop	12
5.	a)	Use k map method to simplify the following functions	$4+4+2=10$
	i)	$F(A,B,C,D) = \pi [M(2,3,4,5,7,8,9,10)]$	
	ii)	$f(m,n,o,p) = \sum \{m(1,2,3,5,7,9,10)\} + d(11,12,13)$	
	iii)	$f(a,b,c) = ab'c + a'b'c' + abc + a'b'c$	
	b)	Use Boolean algebraic techniques to simplify $(xy' + x'y)'(x' + y)$	1
	c)	Use basic gates to draw the logic diagram of $Y = (a+b)'a'b'c$ without changing the function	1
	d)	Use only NOR gate to implement $Y = (a+b'+c)(a+c')$	2
	e)	Design a 2 bit comparator	6
6.	a)	Draw the block diagram of the following	$2 \times 2 = 4$
	i)	4 bit SISO right shift register	
	ii)	2 bit synchronous up counter	
	b)	Why truth table can not be used to design a counter?	3
	c)	Convert the following	3
	i)	Decimal 20 to octal	
	ii)	Hexadecimal A12 into binary	
	iii)	Binary 10.01 into decimal	
	d)	Design a Mod-7 counter using j-k master slave flip flop	10
7.	a)	State De- Morgan's theorems	2
	b)	Distinguish the following	$2+2=4$
	i)	Sequential logic and combinational logic	
	ii)	Edge triggering and pulse triggering of latch	
	c)	Derive the characteristics equations of j-k flip flop	4
	d)	Use only NAND gate to realize $Y = ab' + b'c + ca'$	3
	e)	Write down the function table of the followings	$1.5 \times 2 + 1 + 3 = 7$
		i) 8:1 multiplexer ii) 1:8 De-multiplexer iii) half subtractor ii) BCD to seven segment decoder	