

2022




Linear Integrated Circuits And Systems





Full Marks : 100


Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

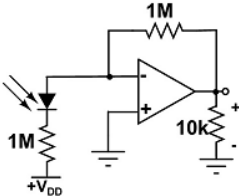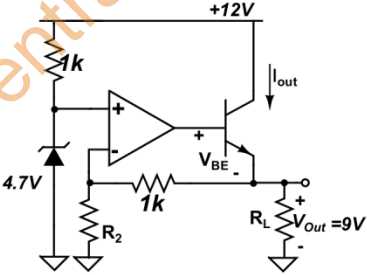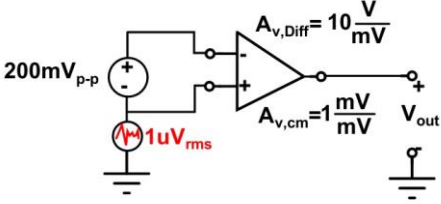1.	<p>a) P-I-N photodiode of responsivity 0.8A/W is connected to the inverting input of an ideal opamp as shown in the figure, $\pm V_{cc} = \pm 15\text{ V}$, Load resistor $R_L = 10\text{ k}\Omega$. If $10\mu\text{W}$ of power is incident on the photodiode, then calculate the value of the photo current through the load.</p> 	6
	<p>b) Draw a opAmp based circuit diagram that can take 2 inputs v_1, v_2 and deliver output voltage of the form of; $v_{out} = \frac{k.T}{q} \ln\left(\frac{v_1}{v_2}\right)$. Explain the mathematical derivations leading to output voltage.</p>	8
	<p>c) Describe the operation of a Schmitt Trigger circuit with waveform and transfer characteristics. Mention the advantages of it with normal comparators.</p>	6
2.	<p>a)</p>  <p>Figure 2 a</p>  <p>Figure 2 b</p> <p>Find the value of the resistor R_2 the BJT used has $V_{BE} = 0.7\text{V}$ and high value of β.</p>	6
	<p>b) An op amp based circuit is shown in Fig. 2 (b). Find the expression for the</p>	2+2 = 4

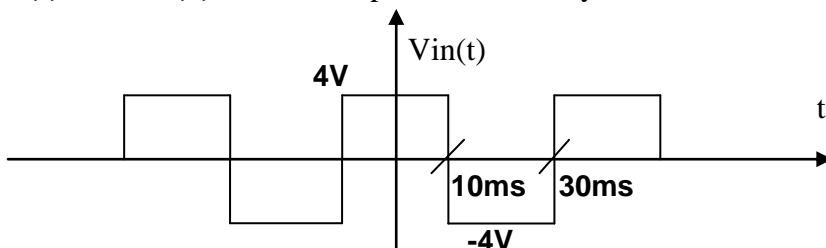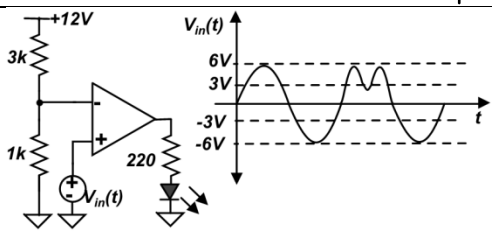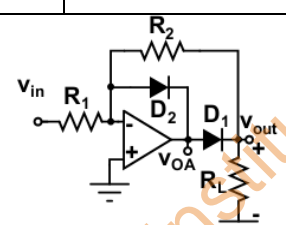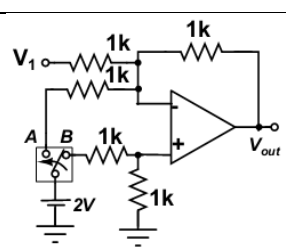		output voltage and CMRR of Opamp in dB?	
	c)	<p>Determine the output waveform from a true integrator for the input waveform as shown, which is governed by the equation: $V_{out}(t) = \int_0^t V_{in}(t) + V_{out}(0)$. Assume capacitor is initially relaxed.</p> 	8
3.	a)	 <p>Draw the output waveform of the comparator and find out the number of times the LED glows assume $\pm 15V$ supply.</p>	8
	b)		$2 \times 2 = 4$
	i)	Draw the circuit diagram of a VCVS whose gain is positive and input resistance is ideally infinite.	
	ii)	Write a short note on input referred offset for an Op-Amp.	
	c)	 <p>Explain the operation of the circuit by taking a sine wave input, draw the waveforms for $V_{in}(t)$, $V_{out}(t)$, $V_{OA}(t)$. Plot the voltage transfer characteristics.</p>	$4+2+2$
4.	a)	Describe the operation of saturated precision rectifier for first quadrant operation with proper circuit diagram and plot the voltage transfer characteristics.	$8+2$
	b)	 <p>For the circuit shown in Figure Output voltage $V_{out} = V_{OA}$ for switch SW</p>	$5+5$

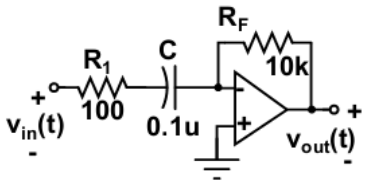		in position A and $V_{out}=V_{oB}$ for SW in position B. Assume that the opamp is ideal. The expression of V_{oA} , V_{oB} .	
5.	a)	Draw the circuit diagram for a 4bit R-2R Digital to Analog Converter and find the value of the output voltage if: $R=10k\Omega$, $R_f=10k\Omega$, $V_{ref}=10V$.	2+4 =6
	b)	Draw the design flow of electronic system.	6
	c)	Derive the expression for the transfer function, plot the gain response vs frequency and find the range frequencies for it can operate as a differentiator.	8
			
6.			
	a)	Draw the circuit diagram of square wave generator in astable mode with an op-amp. Find the expression for the frequency.	10
	b)	Draw the circuit diagram of the difference amplifier with op-amp and derive the expression for the output voltage.	10
7.	a)	Draw the circuit diagram of a Anti-log amplifier with op-amp and derive the expression for the output voltage and mention it's applications in signal processing.	8
	b)	Design a VCVS whose $R_{in}=10k\Omega$, expected gain is $-2V/V$. Find the expression for the output if the input analog signal is $V_{in}(t) = 3\cos 50\pi t + 1.5\sin 300\pi t - 3.5\cos 100\pi t$	8
	c)	Draw the non-ideal model of an op-amp with finite band width and infinite R_{in} and non zero R_{out} .	4