

Total No. of printed pages = 5

19/3rd Sem /UECE515C



2021

LINEAR ICs AND SYSTEM

Full Marks – 100

Time – Three hours

The figures in the margin indicate full marks for the questions.


Answer any *five* questions.

1. (a) Mention at least 5 parameters to be considered while choosing op-amp for a given application. 5
- (b) Implement a current controlled current source using op-amp. 5
- (c) Draw the simplified circuit diagram of 741 op-amp and find the expression for small signal voltage gain. 5+5=10

[Turn over



2. (a)

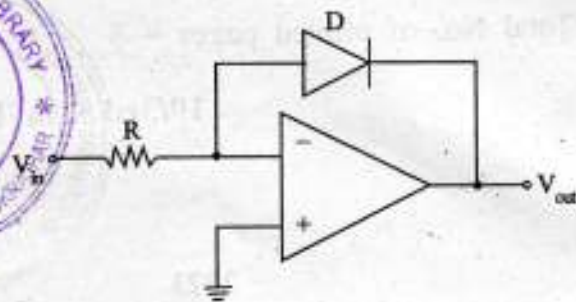


Prove that the output voltage has logarithmic dependence on input voltage. 5

(b) Draw the circuit diagram of an inverting Schmitt trigger circuit and explain its operation and draw the input sine wave and output wave. 10

(c) Draw the circuit diagram for a PWM generator using comparator and explain its operation with input and output waveform. 5

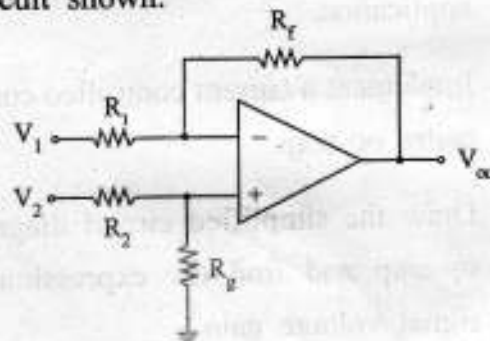3. (a) Find the expression for output voltage in the circuit shown. 10




102/19/3rd Sem/UECE515C

(2)

(b) Cite the differences between Op-amp and comparator. 5


(c) Design a VCVS such that it offers a gain of 10V/V with 10 kΩ input resistance. 5

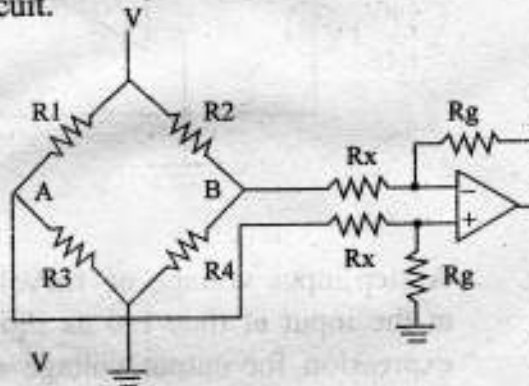4. (a) If $R_1=9.9\text{K}\Omega$, $R_2=11.1\text{k}\Omega$, $R_3=11.1\text{K}\Omega$, $R_4=9.9\text{k}\Omega$, $R_x=1\text{k}\Omega$, $R_f=10\text{k}\Omega$, $V=1\text{V}$, find the output voltage from the following circuit. 5




(b) (i) Explain the operation of windowing comparator with proper diagrams and waveforms. Mention few applications of this circuit. 8+2=10

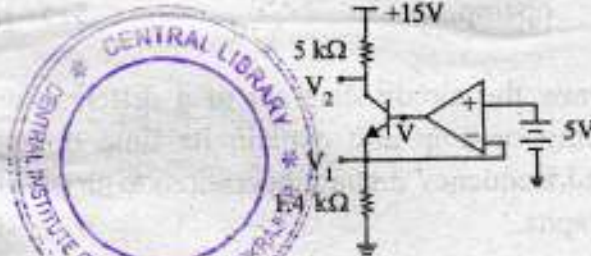(ii) Find the voltage at V_2 and V_1 if $\beta = 100$. 5



5. (a) Explain the operation of a half wave precision rectifier and draw the input and output waveforms. 6

(b)

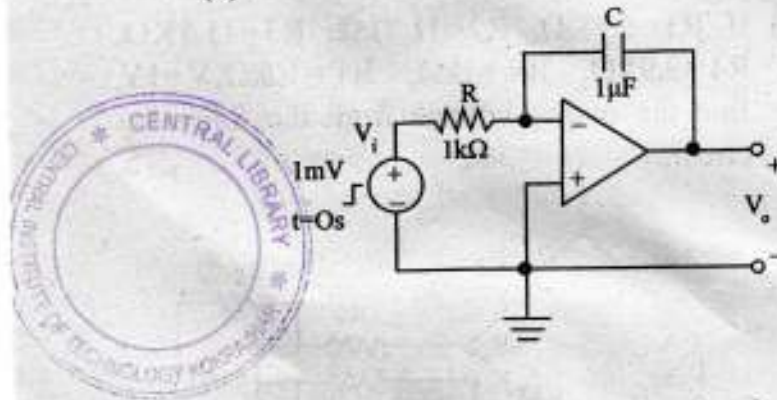

A step-input voltage of 1mVolt is applied at the input at time $t=0$ as shown. Find the expression for output voltage and draw the input and output voltage. 4

- (c) (i) Draw the circuit diagram of an anti-log amplifier and derive the expression for output voltage.
- (ii) Explain the operation of a CCCS using opamp. 5+5=10
6. (a) Draw the circuit diagram of a differentiator using op-amp and explain its time domain and frequency domain operations with proper graphs. 6+4=10

- (b) An operational amplifier is required to amplify a signal with a peak voltage of 5 volts at a frequency of 5 kHz. Find out a slew rate. 5
- (c) Write a short notes on : 5
- (i) CMRR
 - (ii) input offset voltage.

