

2024

Linear Integrated Circuits and Systems

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

1. a) Compare the features of single ended vs differential signaling for electronic systems. [6]
- b) Derive the expression for the output voltage of the following circuit (Fig 1 a) and plot the graph of  $V_{in}$  vs  $V_{out}$ . [8]

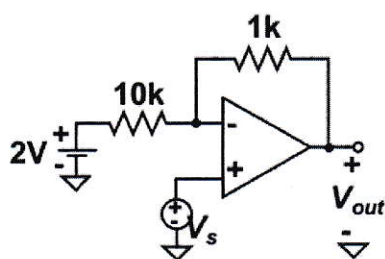


Figure 1 a


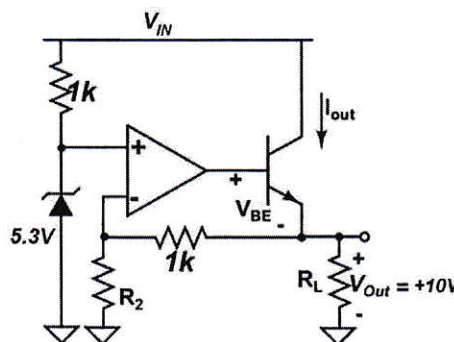


Figure 2 b


- c) Draw the circuit diagram of the precision rectifier. Explain its operation, plot: the input, output voltage and output of op-amp and the voltage transfer characteristics. [6]
2. a) For the voltage regulator circuit shown in Fig 1. (b), the line voltage  $V_{IN} = 20V \pm 20\%$  and regulated output voltage  $V_{OUT}$  is shown. Find the value of the resistor  $R_2$ , and also the maximum power appearing across the  $Q_1$  transistor.  $Q_1$  has  $V_{BE} = 0.7V$  and high value of  $\beta$ . [6+4]
- b) Draw the circuit diagram of a Anti-log amplifier with op-amp and derive the expression for the output voltage and mention its applications in signal processing. [10]
3. a) Describe the operation of a Schmitt Trigger circuit with waveform and transfer characteristics. Mention the advantages of it with normal comparators. [8]
- b) Draw the design flow of electronic system. [4]
- c) Draw the circuit diagram of square wave generator in astable mode with an [8]

op-amp. Find the expression for the frequency.

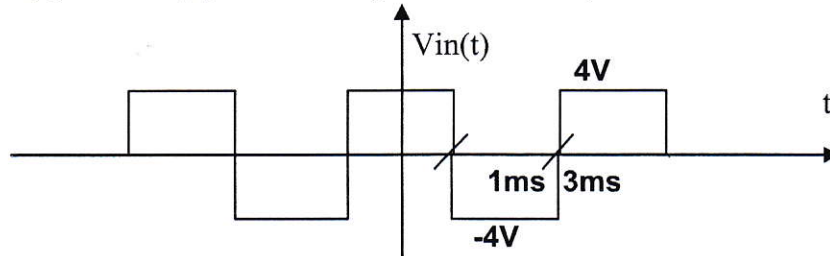4. a) Describe the operation of saturated precision rectifier for first quadrant operation with proper circuit diagram and plot the voltage transfer characteristics. [2+4 =6]
- b) Draw the design flow of electronic system. [6]
- c) Determine the output waveform from a true integrator for the input waveform as shown, which is governed by the equation:  $V_{out}(t) = \int_0^t V_{in}(t) + V_{out}(0)$ . Assume capacitor is initially relaxed. [8]




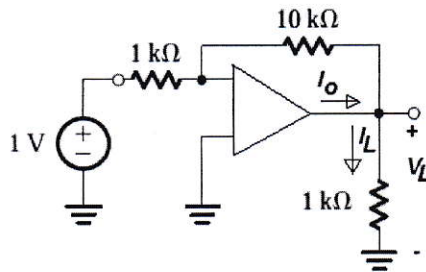5. a) What do you mean by offset voltage? Mention the causes of offset in op-amp. Find the expressions for the input offset voltage of a differential pair. [2+2+6]
- b) Find the values of the output voltage,  $I_o$ ,  $I_L$ ,  $R_{in}$ ,  $R_{out}$  for the circuit shown [10]



here.

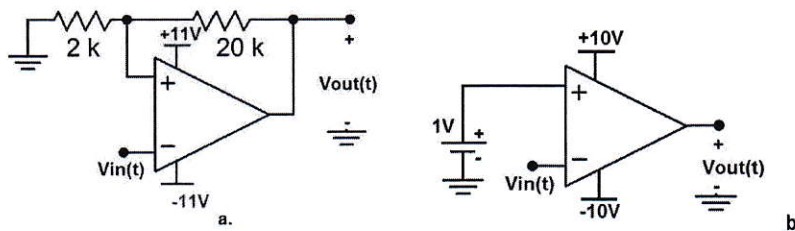6. a) Draw the time domain waveforms:  $v_n(t)$ ,  $v_p(t)$ ,  $v_{out}(t)$ , of the circuit diagram shown below Fig. (a) and plot the voltage transfer characteristics, when it is driven by an input:  $V_{in}(t) = 4V \cos 2000\pi t$ . [8]



- b) Draw the circuit diagram of a VCVS with infinite input impedance. Find the expression for the output of circuit, if the input analog signal is  $V_{in}(t) = 3 \cos 50\pi t + 1.5 \sin 300\pi t - 3.5 \cos 100\pi t$  and  $R_f = 3k\Omega$ ,  $R_1 = 1k\Omega$ . [2+6]
- c) Draw the output of the circuit above Fig (b) and find the duty cycle of the output, while input is 5Vpeak 1kHz sine wave. [4]