

Total number of printed pages: 2 UG/6th /UECE616(B)

2023

POWER ELECTRONICS

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

1.	a)	What is power electronics? Give some applications of power electronics.	2+3=6
	b)	Compare turn off mechanism of TRIAC and Thyristor.	4
	c)	What are the different TURN ON methods of SCR?	3
	d)	Explain the constructional details and working of power MOSFET	7
2.	a)	Define the term holding current and latching current. What is the function of freewheeling diodes in controlled rectifier? Define the delay angle of phase controlled rectifier.	4+3+3=10
	b)	Analyze the constructional details of an SCR. Sketch its schematic diagram and explain its operation.	10
3.	a)	What is Firing Angle? A single phase fully controlled bridge converter with RL load is supplied from 220 V, 50 Hz ac supply. If the firing angle is 45°, determine i) average output voltage, ii) output current iii) input power factor.	3+7=10
	b)	Explain briefly about the different protection required to ensure the reliable operation of power semiconductor device.	10
4.	a)	List a few industrial applications of inverters.	2
	b)	The single phase half bridge inverter has resistive load of R=10 ohm and dc input voltage is 220v. Determine rms output voltage, average value, rms current and output power.	8
	c)	Describe the working of three phase inverter with suitable waveform.	10
5.	a)	What are the advantages and disadvantages of buck/boost regulator?	6
	b)	Draw the schematic diagram of boost converter for the ON and OFF time of switching modes. Discuss in brief why a large capacitor is used in the output of boost converters. Deduce an expression to represent the output	2+2+4=8

	voltage as a function of V_{in} and D .	
c)	A series voltage regulator is required to supply a current of 1A at a constant voltage of 6V. If the supply voltage is 10 V and the Zener operates in the breakdown region, design the circuit. Assume $\beta = 50$, $V_{BE}=0.5V$ and minimum Zener current = 10mA.	6
6.	Write a short notes (<i>any four</i>) on the following: (i) UPS (ii) SMPS (iii) IC voltage regulator (iv) Buck converter (v) Transistor shunt regulator	4×5=20

