

**BASIC ELECTRICAL ENGINEERING**

Course Code: UEE101

Time: 3 Hours

Full Marks: 100

*Answer any five from the following:*

1.


- (a) Find the polar form of  $(-3+4j)$ . Draw the phasor diagram of it. [5]  
 (b) Calculate: [5]

$$\frac{1 + 5.j}{2 - 7.j}$$

- (c) A voltage  $v(t) = 141.4\sin(314t+10^\circ)$  volt is applied to a circuit and a steady current given by  $i(t) = 14.14\sin(314t - 20^\circ)$  Ampere is found to flow through it. Determine (i) the power factor of the circuit (ii) the power delivered to the circuit. [10]

2.

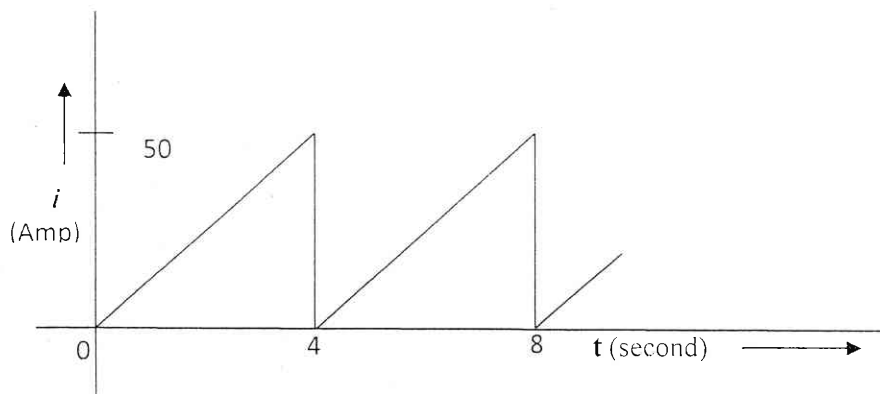- (a) A sinusoidal alternating voltage has an r.m.s. value of 200 Volt and a frequency of 50 Hz. It crosses the zero axis in a positive direction when  $t=0$ . Determine the time when voltage first reaches the instantaneous value of 200 Volt. [5]  
 (b) Find the r.m.s. value of the waveform given in the following figure. [5]




- (c) An impedance of  $(10+j15) \Omega$  is connected in parallel with an impedance of  $(6-j8) \Omega$ . The total current is 15 A. Calculate the currents flowing through individual impedances. Also calculate the total power. [10]

3.




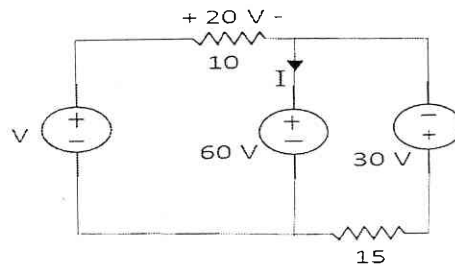- (a) Using KVL and KCL, find the values of  $V$  and  $I$  in the given circuit. All resistances are in ohms. [5]




- (b) State Maximum Power Transfer Theorem. Derive the condition for maximum power transfer. Also write the expression for maximum power. [5]

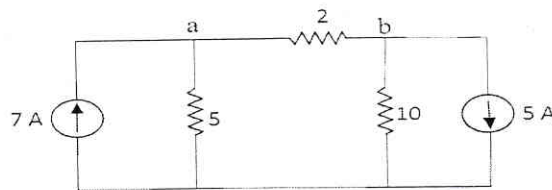- (c) Use Nodal analysis to find various branch currents in the circuit given below. All resistances are in ohm. [10]




4.

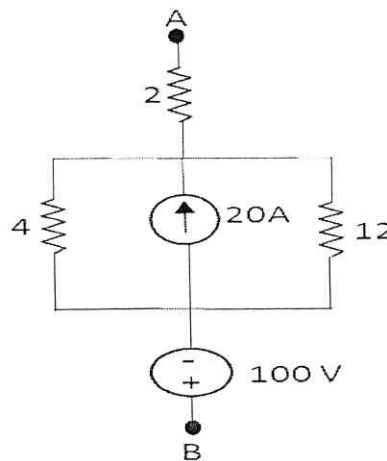
- (a) Find the Thevenin's equivalent resistance as seen from the open-circuited terminals A and B of the circuit shown below. All resistances are in ohms. [5]



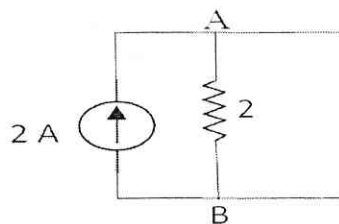- (b) Find the equivalent voltage source for the current source shown below. All resistances are in ohm. [5]



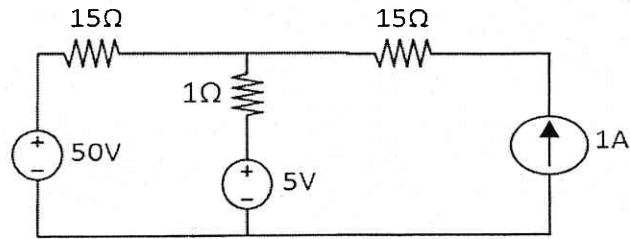(c) Using Superposition Theorem find the branch currents in the circuit given below. [10]



5.

- Find an expression for the deflecting torque of a PMMC instrument. [5]
- What is the importance of fuse in electrical wiring systems? What do you mean by current rating and fusing current of fuse element? [2+1.5+1.5=5]
- A three phase load consists of three similar inductive coils, each of resistance  $50\Omega$  and inductance  $0.3H$ . The supply is  $415V$ ,  $50Hz$ . Calculate (a) the line currents, (b) the power factor, (c) the total power when the load is (i) star connected (ii) delta connected. [5+5=10]

6.

- Write the SI units of the following – [5]
  - Reluctance
  - Permeance
  - Conductivity
  - Specific resistance
  - Admittance
- How will you find the total reluctance of a composite magnetic circuit consists of three different materials with an air gap of  $2\text{ mm}$ . Draw necessary diagrams. [5]
- An iron ring of mean length  $100\text{ cm}$  with an air-gap of  $2\text{ mm}$  has a winding of 500 turns. The relative permeability of iron is 600. When a current of  $3A$  flows in the winding, determine the flux density. [10]

7.

- What are the assumptions of an ideal transformer? Draw the phasor diagram of an ideal transformer on no load. Derive an expression for the emf equation of a single phase transformer. [3+3+4=10]
- A single phase  $50Hz$  transformer has 20 primary turns and 273 secondary turns. The net cross sectional area of the core is  $400\text{ cm}^2$ . If the primary winding is connected to  $230V$  supply, find (i) peak value of flux density in the core (ii) voltage induced in the secondary winding. [10]

