

Total No. of printed pages = 5

19/6th Sem/UIE 602

2022

ELECTRONIC INSTRUMENTATION

Full Marks - 100


Time - Three hours

The figures in the margin indicate full marks for the questions.


Answer any five questions.

1. (a) Explain how does a PMMC type DC ammeter work? A rectifier ammeter as shown below gives Full Scale Deflection (FSD) for a primary current of 250 mA. The PMMC meter has $FSD = 1\text{mA}$ and $R_m = 1700\Omega$. The current transformer has $N_s = 500$ and $N_p = 4$. If each of the diodes have $V_F = 0.7\text{V}$ and series resistance $R_s = 20\text{ k}\Omega$, calculate the required value of R_L .

4+6=10

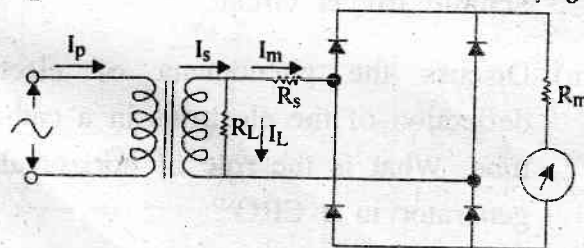

[Turn over

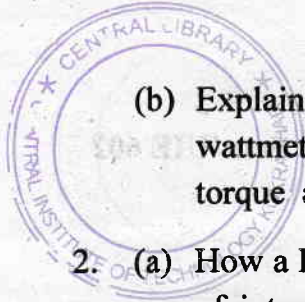


- (b) Explain the working of induction type wattmeter and derive the relationship between torque and power. 10
2. (a) How a RF signal can be converted to a signal of intermediate frequency? Describe how a true RMS value of a signal can be obtained by using thermocouple? Explain the working of an LCR meter. 2+3+5=10
- (b) What are the Barkhausen criteria for the generation of oscillating signal? Explain the working of phase locked loop for synthesizing desired frequency. 2+8=10
3. (a) What happens to the capacitance of a varactor diode, when the applied reverse biased voltage is increased? Describe how a voltage controlled oscillator works? 2+4=6
- (b) Explain how square wave signals can be generated? Illustrate the operation of a Schmitt trigger circuit. 7+7=14
4. (a) Discuss the phenomena of electrostatic deflection of the electrons in a cathode ray tube. What is the role of horizontal sweep generator in a CRO?

A 500 Hz triangular wave with a peak amplitude of 40V is applied to the vertical deflecting plates of a CRT. A 250 Hz sawtooth wave with a peak amplitude of 50V is applied to the horizontal deflecting plates. The CRT has a vertical deflection sensitivity of 0.1 cm/V and a horizontal deflection sensitivity of 0.08 cm/V. Assuming that the two inputs are synchronized, determine the waveform displayed on the screen.

$$2+2+8=12$$

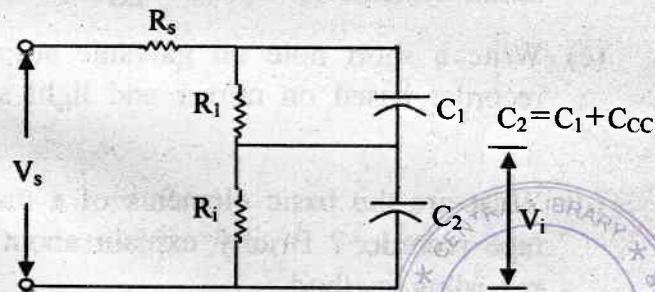- (b) Draw the circuit of 10 :1 oscilloscope probe by distinguishing signal source, probe and oscilloscope part of the circuit.


Calculate the value of C_1 required to a 10 :1 probe when the oscilloscope input capacitance is 30 pF and the coaxial cable capacitance is 100 pF. Also calculate the probe input capacitance seen from outside. $3+5=8$



115/19/6th Sem/UIE 602

(3)

[Turn over

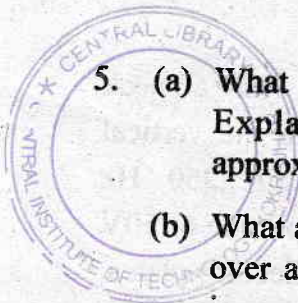

5. (a) What is quantization error of an ADC ? Explain the working of successive approximation type ADC. $2+5=7$
- (b) What are the advantages of digital multimeter over analog multimeter ? A 20V DC voltage is measured by analog and digital multimeters. The range of the analog instrument is 25V and its specified accuracy is $\pm 2.5\%$. The digital meter has $3\frac{1}{2}$ digit display and accuracy of $\pm(0.6+1)$. Determine the measurement accuracy of the two meters. $2+3=5$
- (c) With the help of a block diagram describe the working principle of digital frequency meter. 8
6. (a) How is bar graph display different from dot matrix display ? — Explain. 3
- (b) What is a data logger ? What are the different standard protocols for connecting instrumentation systems to a data logger ? $2+1=3$
- (c) Write a short note on galvanic strip chart recorder based on mirror and light source. 6
- (d) What are the basic elements of a magnetic tape recorder ? Briefly explain about direct recording method. $3+5=8$

7. Write short notes on any *four* of the following :

5×4=20

- (i) Vector voltmeter
- (ii) Sweep frequency generator
- (iii) Heterodyne harmonic analyzer
- (iv) Digital storage oscilloscope
- (v) Digital frequency meter
- (vi) X-Y recorder.

