

2022

NETWORK THEORY


Full Marks: 100

Time: Three hours


The figures in the margin indicate full marks for the questions.

Answer any five questions.

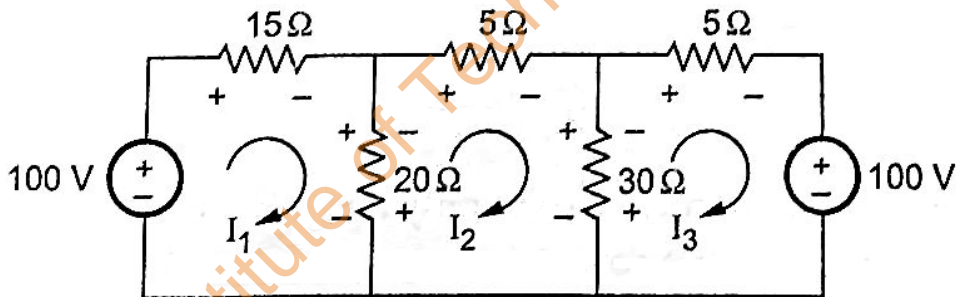1. a) Differentiate the following network elements: 2+2=4
 (i) Linear and Non-linear
 (ii) Active and passive
- b) For the circuit shown in the figure below find the current through 30Ω resistance using mesh analysis 6




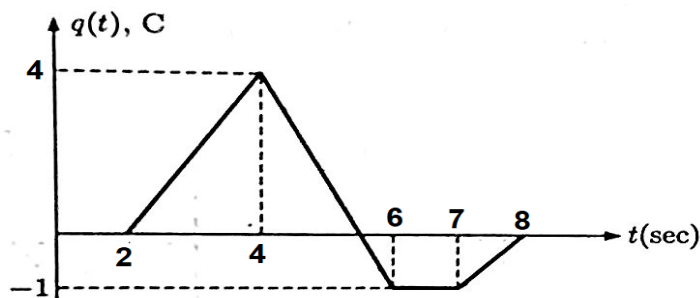- c) The charge flowing in a circuit element is plotted in the following figure. 8
 Draw the plot for current $i(t)$




- d) Explain various dependent sources. 2

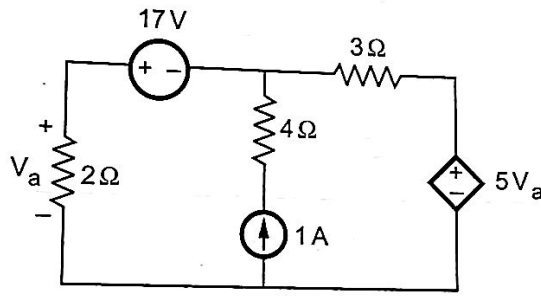
2. a) Find V_a using Superposition principle in the circuit shown below 6



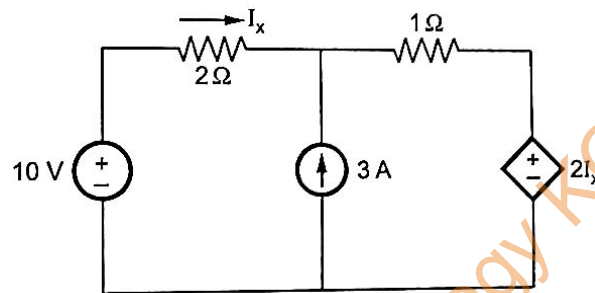
- b) Obtain the current I_x by Thevenin's theorem. 8



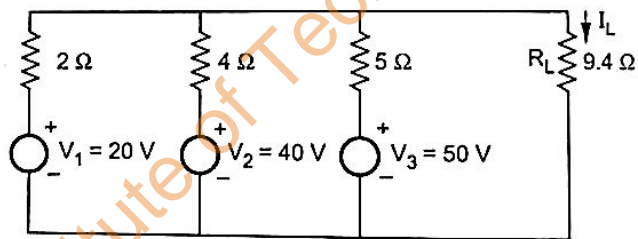
- c) Using Millman's theorem find I_L through R_L for the network shown below. 6



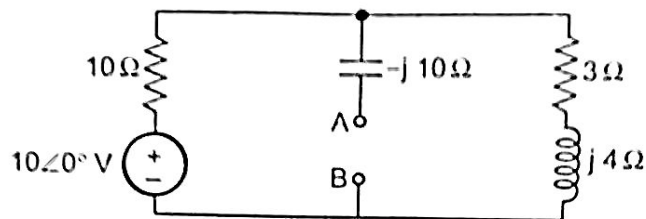
3. a) Replace the network at terminals AB with Norton's equivalent circuit. 8



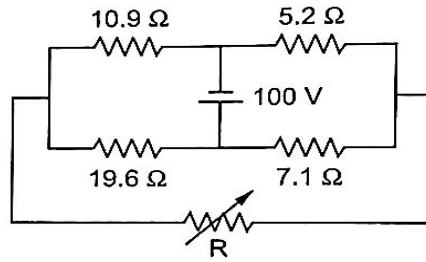- b) For the following given circuit find the value of R that will receive maximum power. 8




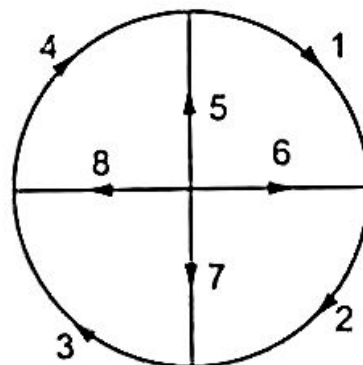- c) State and explain reciprocity theorem. 4
4. a) Define following terms: 3
 (i) Q factor (ii) Bandwidth (iii) Selectivity
- b) Show that resonant frequency of series resonance circuit is equal to the geometric mean of two half power frequencies. 7
- c) It is required that a series RLC circuit should resonate at 1 MHz. Determine values of R,L and C if bandwidth of the circuit is 5 kHz and its impedance is 50Ω at resonance. 6
- d) Explain the properties of RLC series resonant circuit. 4
5. a) Distinguish the following 4
 (i) Oriented and unoriented graph
 (ii) Planner and non-planner graph
- b) For the graph shown below write tie set and cut set matrices with chords (4,5,2,8) 10



c) Construct dual network of the circuit shown below.

6

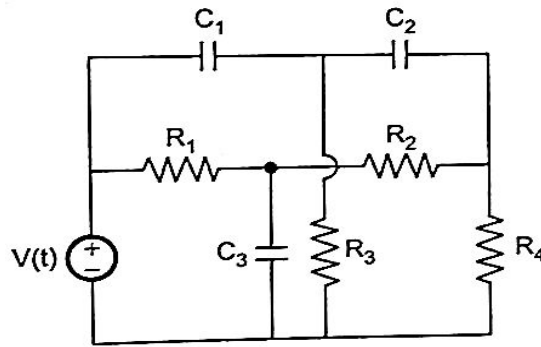


6 a) Use initial and final value theorems to find $f(0)$ and $f(\infty)$

4

$$F(s) = \frac{s^3 + 7s^2 + 5}{s^4 + 3s^3 + 4s^2 + 2s}$$


b) In the network shown below the switch K is moved from position 'a' to 'b' at $t=0$ (a steady state existing in position 'a' before $t=0$). Solve for the current $i(t)$, using Laplace Transformation.

6

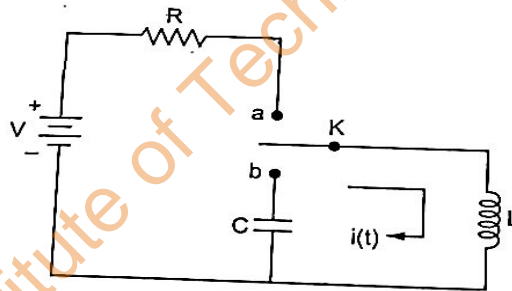


c) In the network shown switch K is closed at $t=0$, with the capacitor uncharged. Find the values for $i(0^+)$, $di(0^+)/dt$, and $d^2i(0^+)/dt^2$.

10

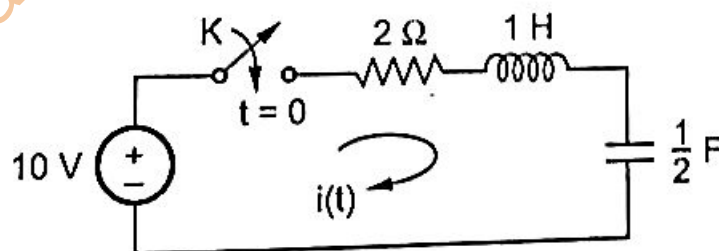

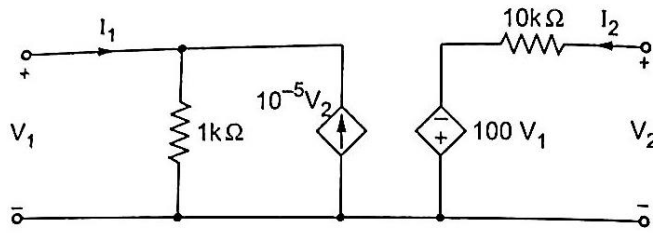- 7 a) Define Z and Y parameters. 4
- b) Find Z parameter for the following circuit. 10



- c) Establish a relationship between line and phase voltages and currents in a star connection. 6

Central Institute of Technology KOkrajhar