

2023

NETWORK THEORY


Full Marks: 100

Time: Three hours


The figures in the margin indicate full marks for the questions.

Answer any five questions.

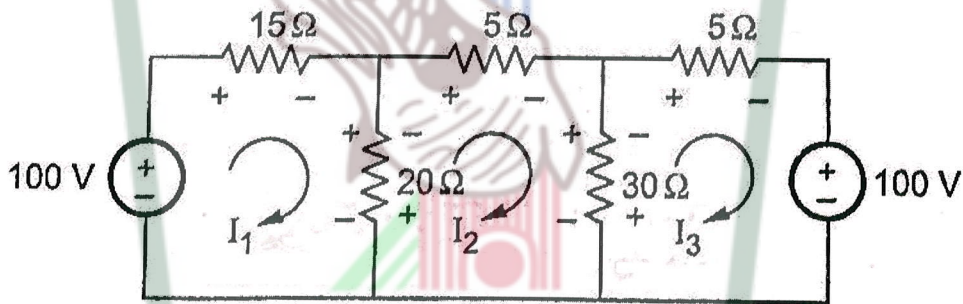1. a) Define the following: 4
 (i) Active element (ii) Bilateral element (iii) Lumped network
 (iv) Continuous system
- b) For the circuit shown in the figure below find the current through 30Ω resistance using mesh analysis. 6




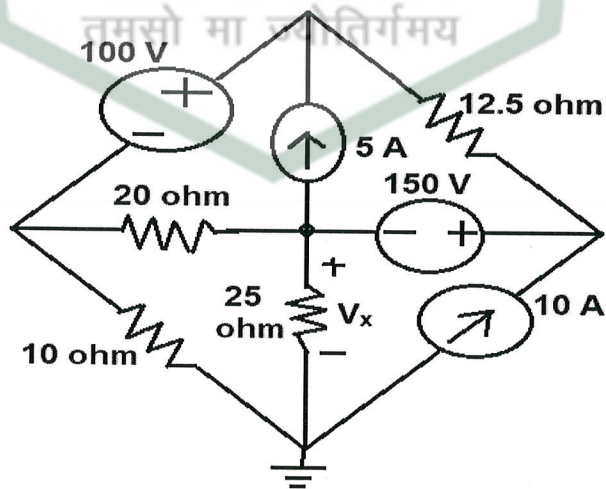- c) Find V_x using nodal analysis for the network shown below. 10




[Turn Over]

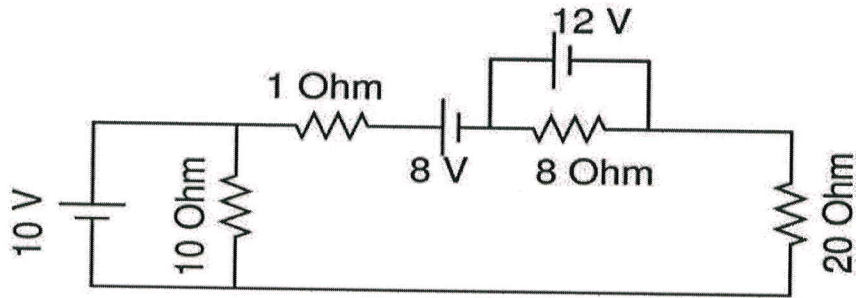
2. a) Find the current through $20\ \Omega$ resistor using Superposition principle in the circuit shown below. 10



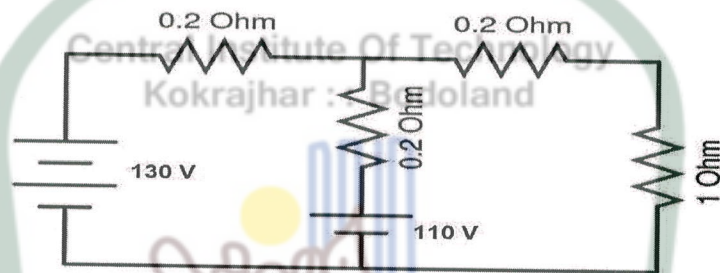
- b) Find current flowing through $1\ \Omega$ resistor by Thevenin's theorem in the circuit shown below. 7



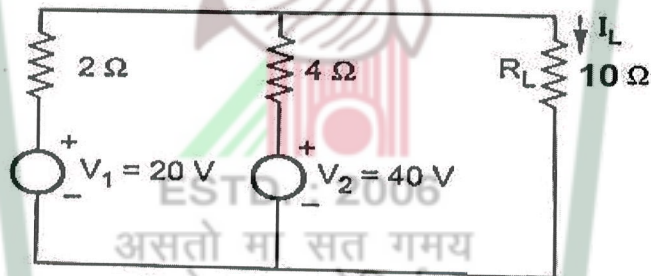
- c) Using Millman's theorem find I_L through R_L for the network shown below. 3



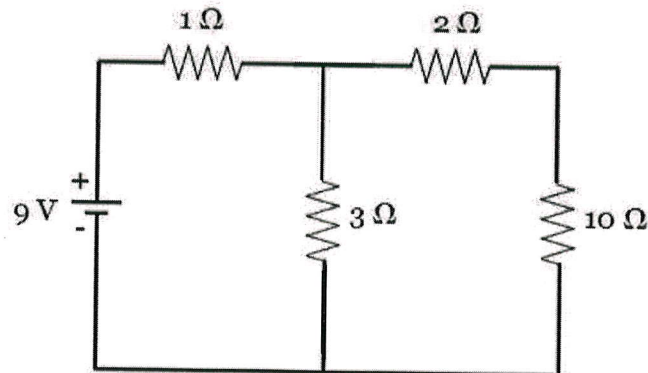3. a) For the given circuit, determine the current flowing through $10\ \Omega$ resistor using Norton's theorem. 8



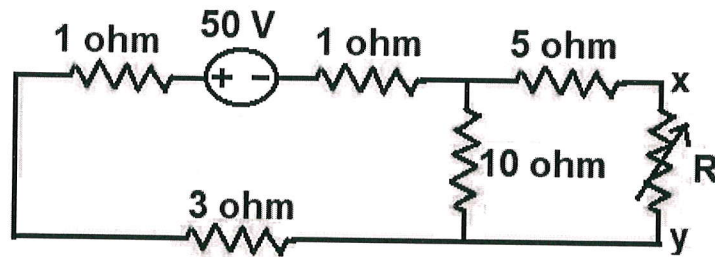- b) Find maximum power delivered to the load R in the given circuit. 8



- c) State and explain reciprocity theorem. 4

4. a) Define following terms: 3

(i) Resonance (ii) Bandwidth (iii) Half power frequency

- b) Show that resonant frequency of series resonance circuit is equal to the geometric mean of two half power frequencies. 8


- c) A series RLC circuit consist of a resistance of $1\text{ k}\Omega$ and an inductance of 100 mH in series with capacitance of 10 pF . If 100 V is applied as input across the combination determine (i) Resonant frequency (ii) Maximum current in the circuit (iii) Q-factor of the circuit (iv) Half power frequencies. 6

- d) Draw the resonance curve of the series RLC circuit. 3

5. a) Define the following terms: 4

(i) Oriented graph (ii) Non-planner graph (iii) Twig (iv) Subgraph

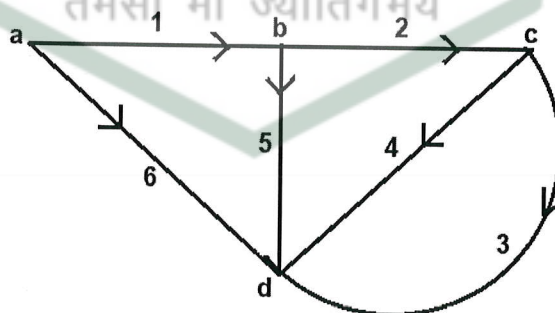
- b) For the graph shown below write tie set matrix with twigs (4, 5, 6). 5



- c) What are the properties of a tree in graph theory? 5

d) Construct dual network of the circuit shown below.

6

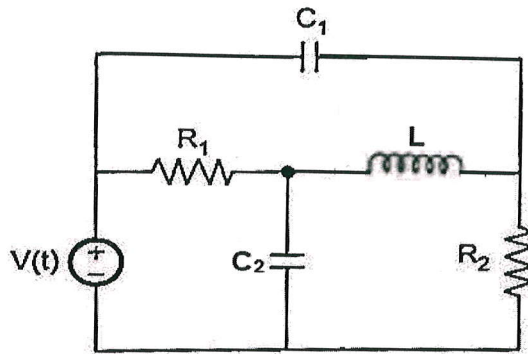


6 a) Define initial and final value theorems.

4

b) In the network shown below the switch K is moved from position 'a' to 'b' at $t=0$ (a steady state existing in position 'a' before $t=0$). Solve for the current $i(t)$, using Laplace Transformation.

6

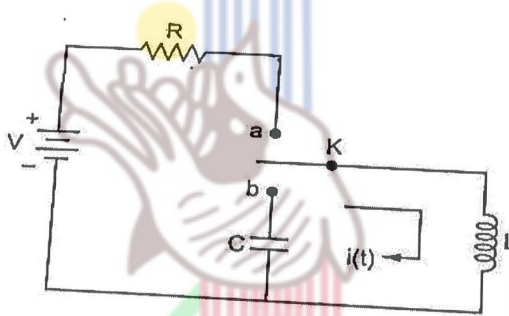

c) Find the transient response of a driven series R-L circuit.

10

7 a) Define T parameters.

असतो मा सत गमय

2

b) Express Y parameters in terms of Z parameters.

तमसो मा ज्योतिर्गमय

7

c) A two port network has the following Z-Parameters: $Z_{11}=10 \Omega$, $Z_{22}=12 \Omega$, $Z_{12}=Z_{21}=5 \Omega$. Compute the Y-parameters for the same network.

5

d) Establish a relationship between line and phase voltages and currents in a star connection.

6
