

2022

Electronic Devices and Circuits

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

1.	a)	Derive the expression for density of states function of a cubic crystal with lattice constant 'a'.	10
	b)	Derive the expression for thermal equilibrium electron concentration in the conduction band of an N-type semiconductor	10
2	a)	Derive the expression for Fermi Dirac distribution function.	10
	b)	Define Fermi level and explain how Fermi level is positioned in intrinsic, N-type and P-type semiconductor.	5
	c)	Derive the Einstein's equation for diffusion.	5
3.	a)	Derive the built-in potential expression of a p-n junction under zero bias.	10
	c)	Derive the expression for depletion width of a p-n junction under zero bias.	10
3.	a)	Explain the working of half wave and fullwave rectifiers with neat diagram	8
	b)	Draw the circuit diagram and output waveforms of Positive simple series clipper and Positive biased series clipper	6
	c)	Given the load line of Fig. 1 and the defined Q -point, determine the required values of VCC , RC , and RB for a fixed-bias configuration.	6

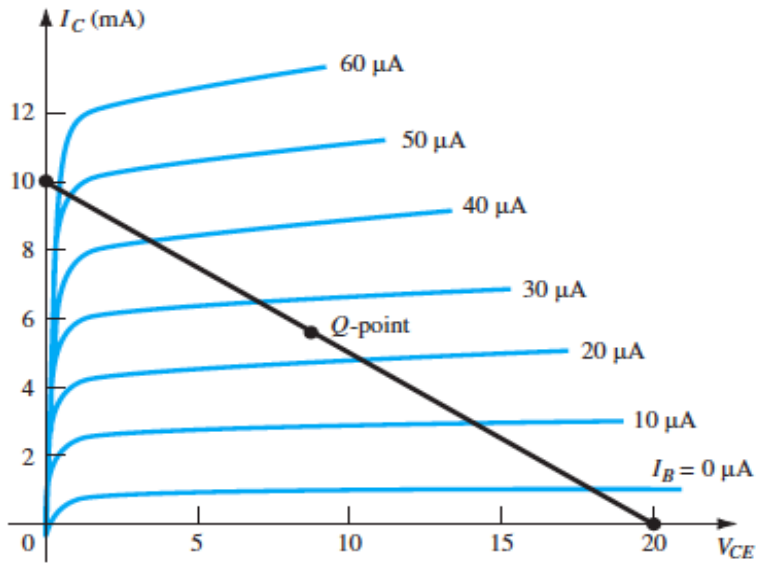


Fig. 1

4. a) For the emitter-bias network of Fig. 2 , determine:

- a. I_B .
- b. I_C .
- c. V_{CE} .
- d. V_C .
- e. V_E .
- f. V_B .
- g. V_{BC} .

14

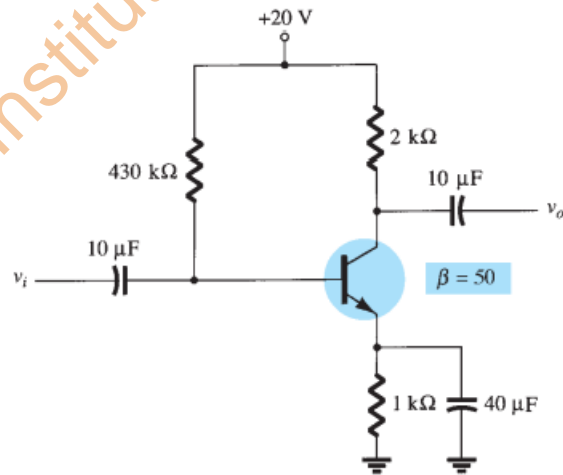


Fig.2

b) Determine the dc bias voltage V_{CE} and the current I_C for the voltage divider configuration of Fig. 3 .

6

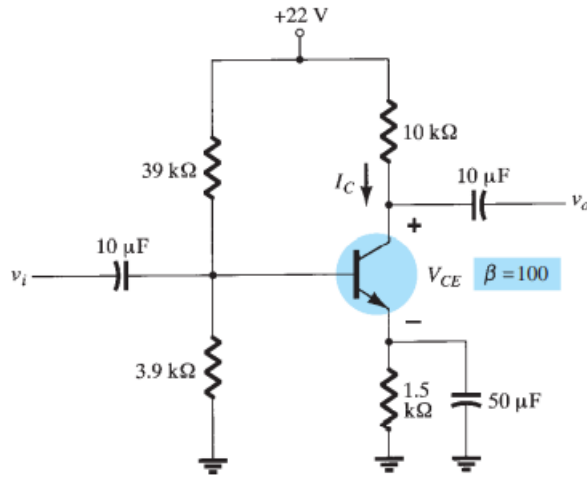
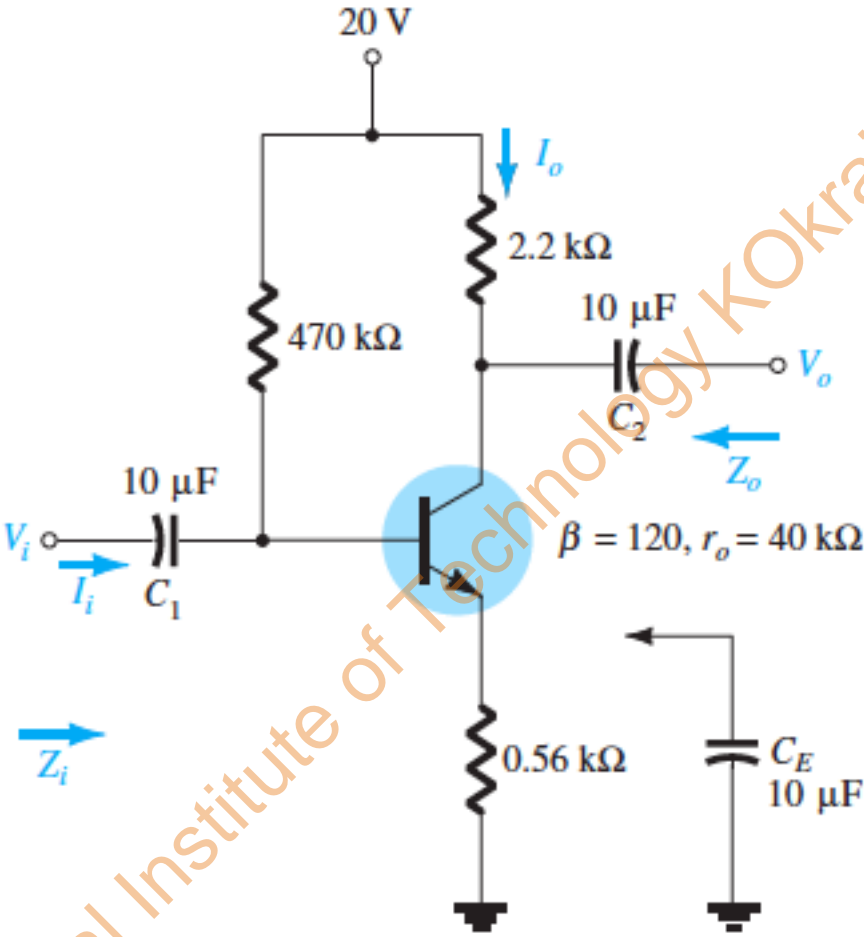


Fig. 3

5

a) Derive the expressions for input impedance, output impedance and voltage gain of Common Emitter fixed bias and voltage divider bias configurations

14

	<p>b) For the network of Fig. 4 , without C_E (unbypassed), determine:</p> <ol style="list-style-type: none"> r_e . Z_i . Z_o . A_v .  <p style="text-align: center;">Fig. 4</p>	6
6.	<p>a) Determine the following for the network of Fig. 5:</p> <ol style="list-style-type: none"> V_{GSQ} . I_{DQ} . V_{DS} . V_D . V_G . V_S . 	6

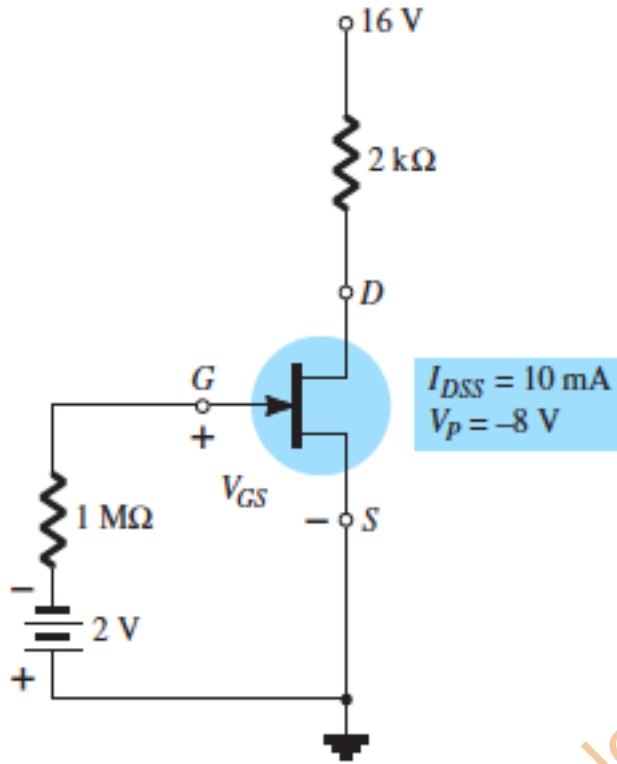


Fig. 5

b) Determine V_{DS} for the network of Fig. 6.

4

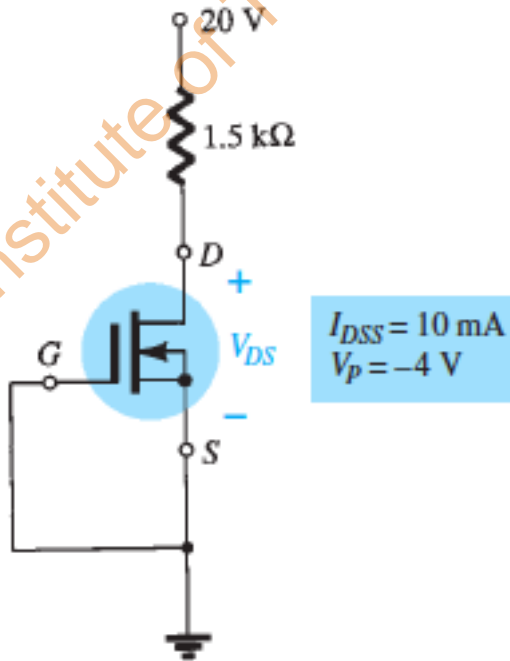


Fig. 6

c) Explain the feedback biasing and voltage divider biasing of Enhancement type MOSFET

10

7. a) Derive the expressions for gain for voltage series and voltage shunt

6+6=12

	feedback	
b)	Determine the maximum efficiency of a series fed class A amplifier	8

Central Institute of Technology KOkrajhar