

Total number of printed pages: 5

Programme(UG)/Semester/UIE302

2023

Electronic Devices and Circuits


Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.


Answer any five questions.

1.	a)	Derive the expression for density of states function of a cubic crystal with lattice constant 'a'.	10
	b)	Derive the expression for Fermi Dirac distribution function.	10
2.	a)	Derive the expression for thermal equilibrium electron concentration in the conduction band of an N-type semiconductor	8
	b)	Derive the expression for space charge width of an abrupt pn junction under zero bias condition.	7
	c)	State and explain Hall effect in Semiconductor	5
3.	a)	Define static and dynamic resistance of a diode. Obtain the expression for ac resistance of a diode at room temperature.	10
	b)	What is load line? Draw and explain the concept of load line of a diode.	4
	c)	Draw the circuit diagram and output waveforms of Positive simple series clipper and Positive biased series clipper	6
4.	a)	Determine the following for the fixed-bias configuration of Fig. 1 i. IBQ and ICQ. ii. VCEQ. iii. VB and VC . iv. VBC .	8

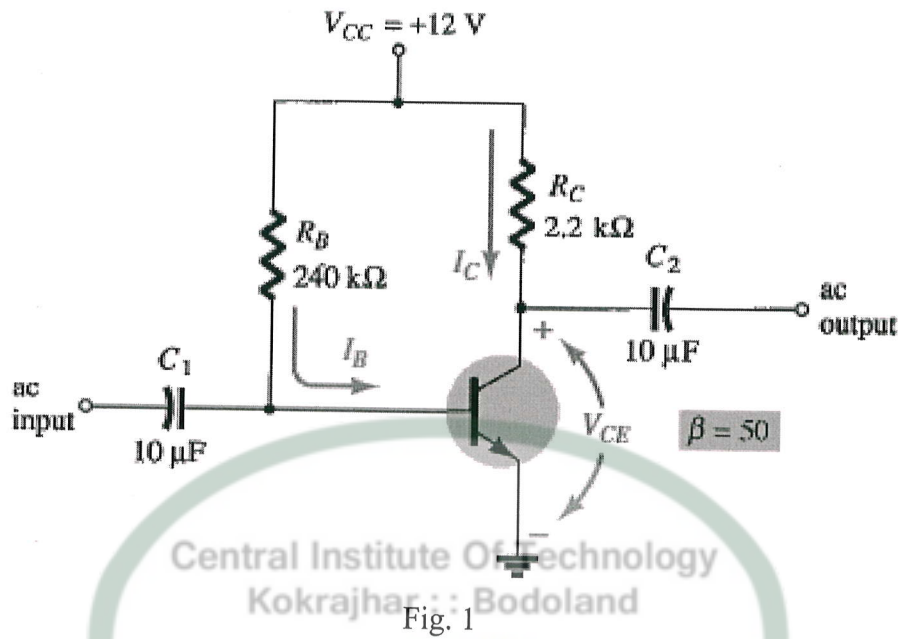

- b) Given the load line of Fig. 2 and the defined Q -point, determine the required values of V_{CC} , R_C , and R_B for a fixed-bias configuration.

6

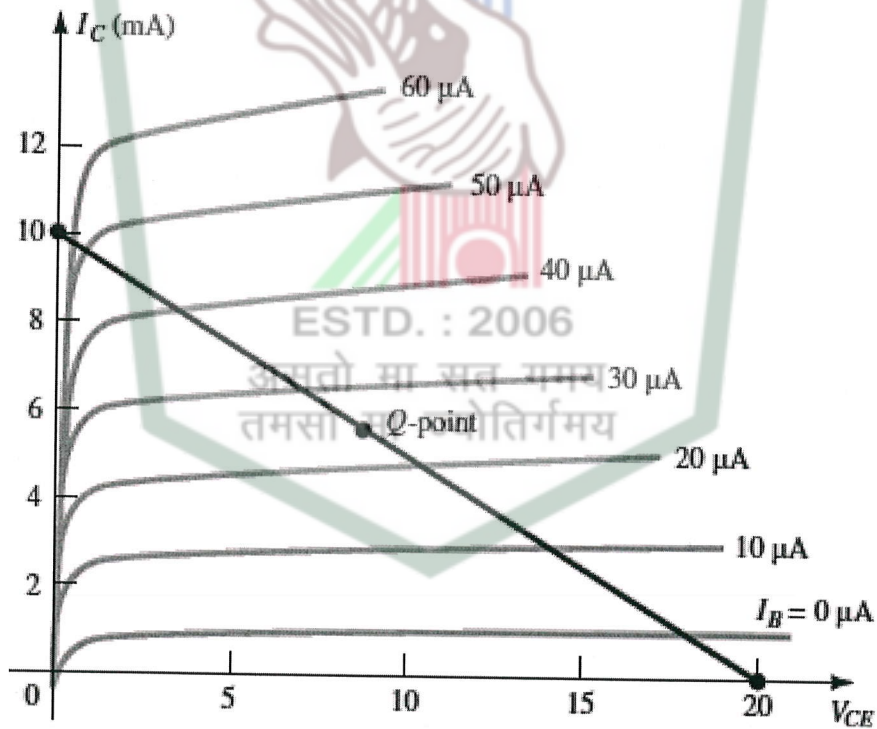

- c) For the network of Fig. 3 :
- Determine r_e .
 - Find Z_i (with $r_o = \infty$).
 - Calculate Z_o (with $r_o = \infty$).
 - Determine A_v (with $r_o = \infty$).
 - Repeat parts (c) and (d) including $r_o = 50 \text{ k}$ in all calculations and compare results.

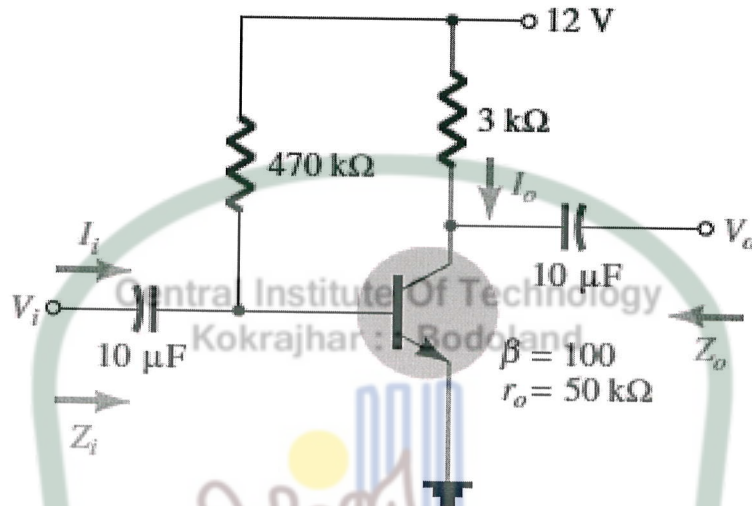


Fig. 3

- 5 a) For the network of Fig. 4, without CE (unbypassed), determine:
- r_e .
 - Z_i .
 - Z_o .
 - A_v .

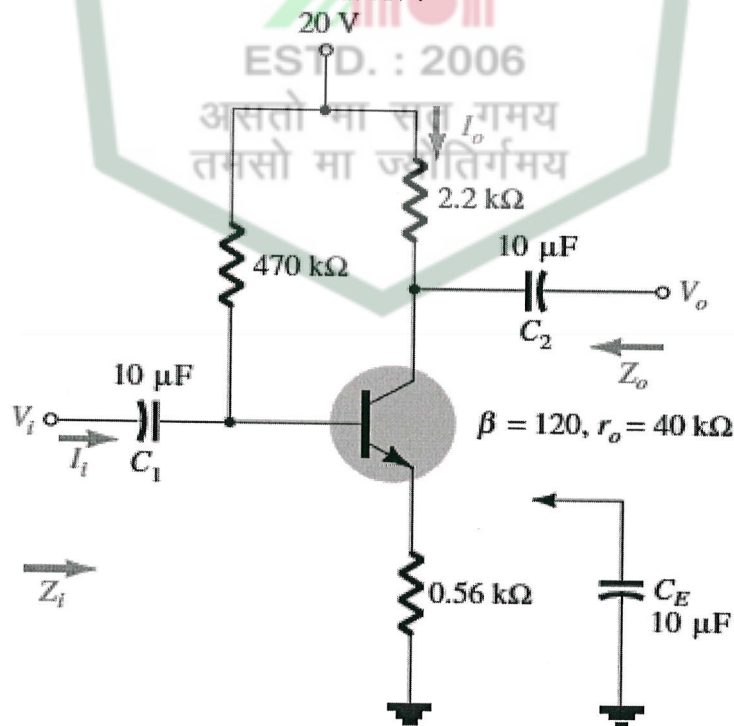


Fig. 4

- b) Determine the following for the network of Fig. 5:
- V_{GSQ} .
 - I_{DQ} .
 - V_{DS} .
 - V_D .
 - V_G .
 - V_S .

7

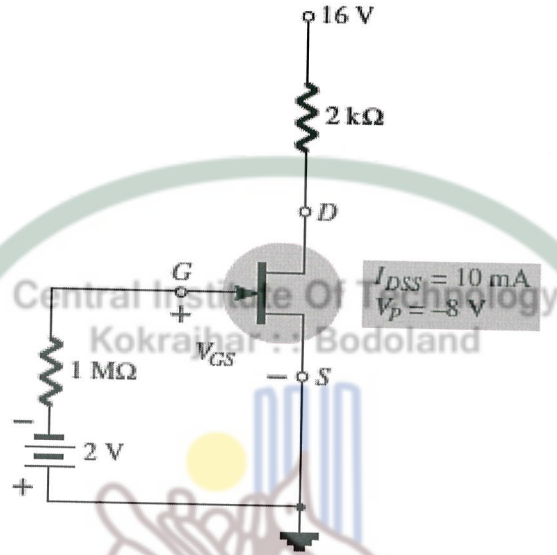


Fig. 5

- c) Determine V_{DS} for the network of Fig. 6.

5

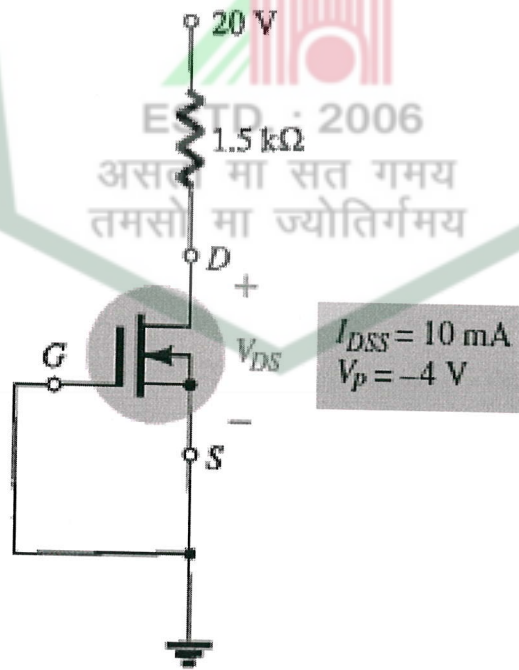
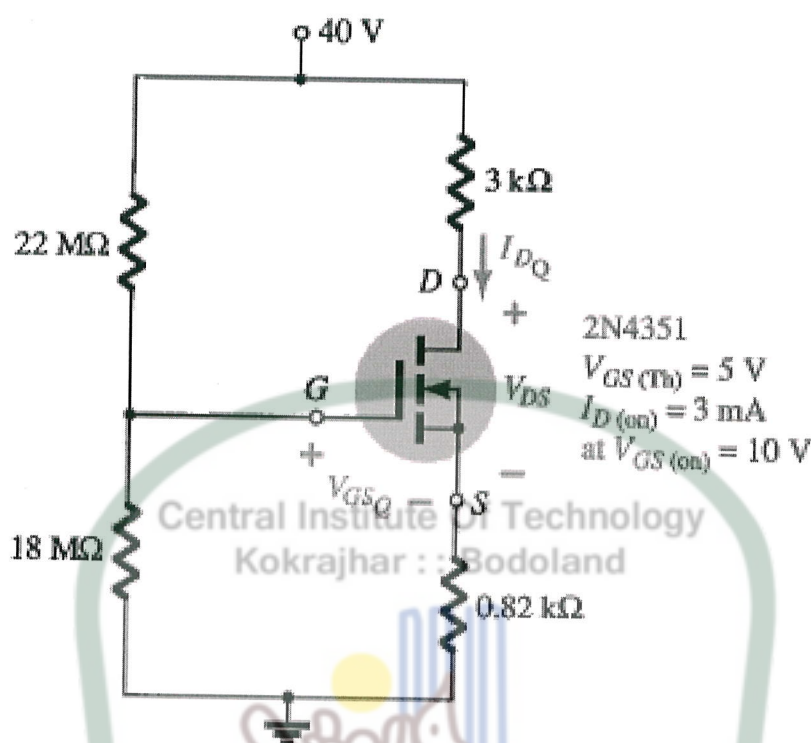


Fig. 6

6	<p>a) Determine I_{DQ}, V_{GSQ}, and V_{DS} for the network of Fig. 7.</p>  <p>Fig.7</p>	10
	<p>b) Calculate the efficiency of a transformer-coupled class A amplifier for a supply of 12 V and outputs of:</p> <ol style="list-style-type: none"> $V(p) = 12$ V. $V(p) = 6$ V. $V(p) = 2$ V 	6
	<p>c) For a class B amplifier providing a 20-V peak signal to a 16 ohm load (speaker) and a power supply of $V_{CC} = 30$ V, determine the input power, output power, and circuit efficiency.</p>	4
7	<p>a) Derive the expressions for gain for voltage series and voltage shunt feedback</p>	5+5=10
	<p>b) Determine the maximum efficiency of a Class B amplifier.</p>	10