

2023

ELECTRICAL AND ELECTRONIC MEASUREMENTS

Full Marks: 100

Time: Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

Symbols have their usual significances.

- 1 a) How power is measured in a three phase system using wattmeters? Explain using diagrams. 7
- b) The phase voltage and current of a star-connected load is 230 V and 15 A. The power factor of load is 0.707 (lag). Assuming that the system is 3-wire and power is measured using two wattmeters, find the readings of wattmeters. 6
- c) What are the possible causes of error in an electrodynamicometer wattmeter? Explain 7
- 2 a) Describe the construction and working of single phase energy meter using a suitable diagram. 10
- b) A meter constant of a single phase induction type energy meter is 720 revolutions per kWh. Calculate the load in kW if the meter makes nine revolutions in 30 seconds. 4
- c) How energy meters are tested using long period dial test? Explain using a diagram. 6
- 3 a) How the following parameters are measured using AC bridges? 7 + 7 = 14
(i) Inductance, and (ii) Frequency
Explain using suitable diagrams and relevant mathematical relations.
- b) The four arms of a bridge are:
Arm AB, consist of a capacitor of $0.4\mu\text{F}$ in parallel with $1\text{k}\Omega$ resistance,
Arm BC, consist of a capacitor of $0.6\mu\text{F}$,
Arm CD, consist of an unknown resistance in series with an unknown capacitor and
Arm DA, consist of a resistance of $300\ \Omega$.
Determine the unknown capacitance and dissipation factor. 6
- 4 a) Explain the deflecting force, controlling force and damping force 6

- b) Explain, with the schematic diagram, the principle of operation of permanent magnet moving coil (PMMC) instrument. 10
- Mention their advantages and disadvantages. 4
- 5 a) Explain, with the schematic diagram, the principle of operation of attraction type moving iron (MI) instrument. 10
- Mention their advantages and disadvantages. 4
- b) The inductance of a moving iron instrument is given by $L = 10 + 5\theta - \theta^2 \mu H$, where θ is the deflection in radian from zero position. The spring constant is $12 \times 10^{-6} Nm/rad$. Estimate the deflection for a current of 5A. 6
- 6 a) What are the methods for low resistance measurements? 2
- b) Draw and explain the principle of operation of Kelvin Double Bridge method for low resistance measurement. 16
- Why is it called “double bridge”? 2
- 7 Write short notes on any two of the following 10x2=
- a) Extension of PMMC instrument as ammeter and voltmeter connection
- b) Ammeter Voltmeter method
- c) Loss of charge method for high resistance measurement
- d) Current measurement using DC potentiometer 20

ESTD. : 2006
 असतो मा सद्गमय
 तमसो मा ज्योतिर्गमय