


ANALOG INTEGRATED CIRCUITS

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.
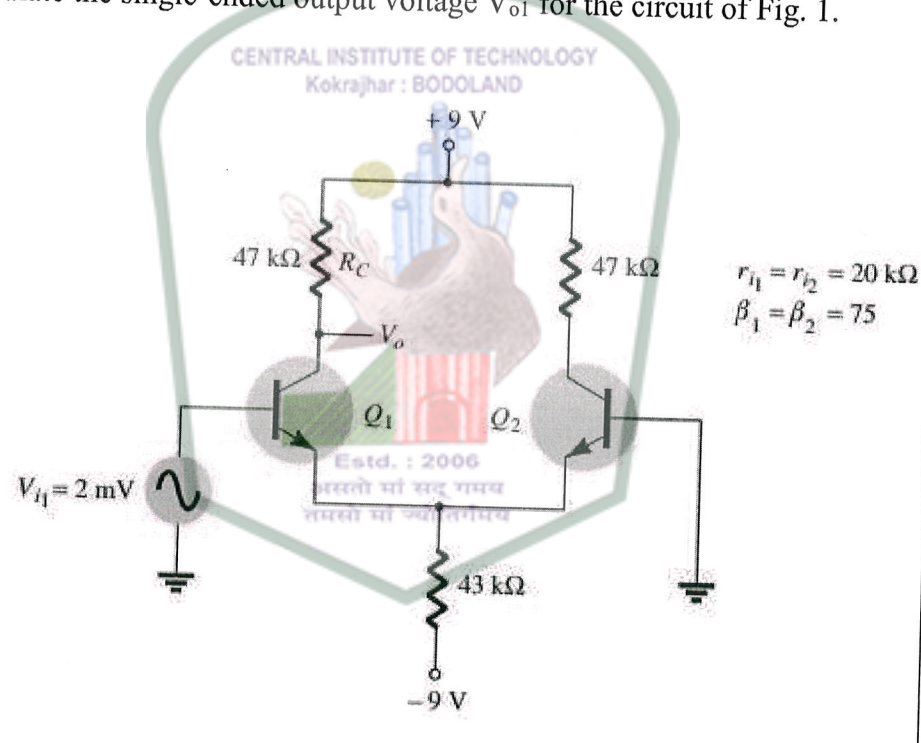
<p>1. a)</p>	<p>Calculate the single-ended output voltage V_{o1} for the circuit of Fig. 1.</p>  <p style="text-align: center;">Fig.1</p>	<p>6</p>
<p>b)</p>	<p>Derive the expressions for gains of OPamp based inverting and non-inverting amplifier.</p>	<p>10</p>
<p>c)</p>	<p>A non-inverting operational summing amplifier is shown in fig. 2 Find V_o.</p>	<p>4</p>

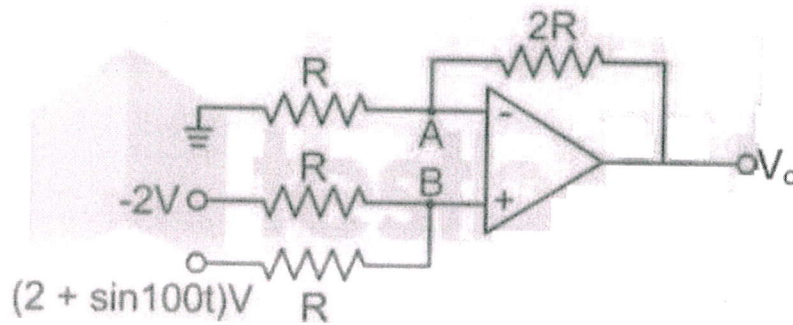


Fig.2

2. a) What are the different types of controlled sources using OpAmp. Explain each type.

10

b) In the circuit shown the saturation voltage $\pm 15V$ and the input voltage is $-3.5V$. Find the output voltage.

5

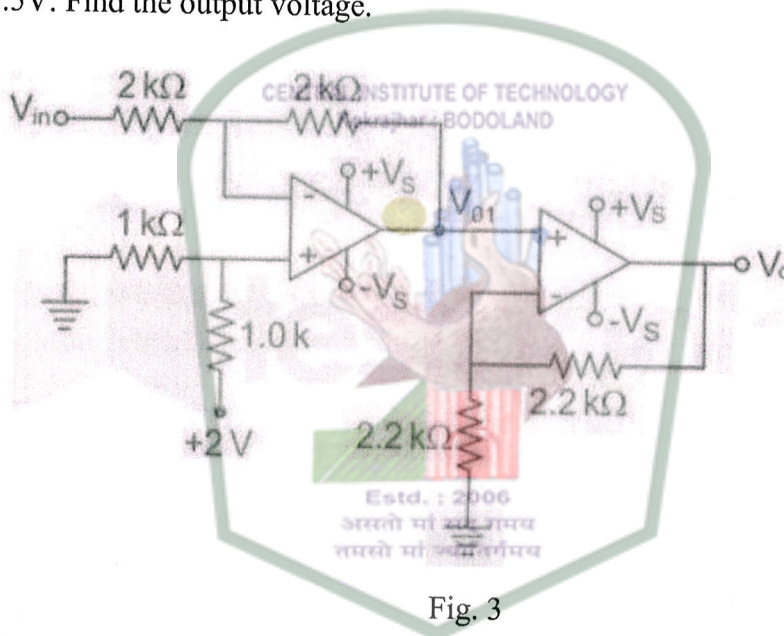


Fig. 3

c) For the operational amplifier circuit shown, the output saturation voltages are $\pm 15V$. The upper and lower threshold voltages for the circuit are, respectively.

5

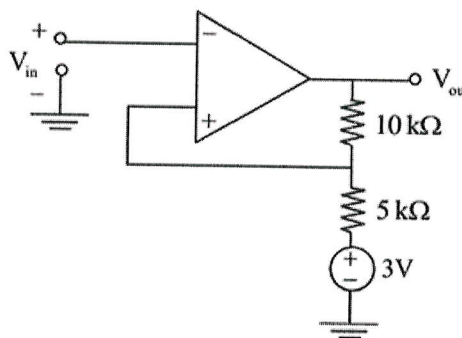
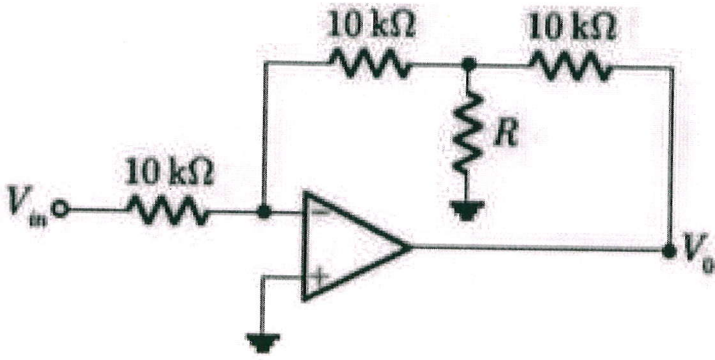


Fig. 4

3. a) In the circuit of Fig. 5 assume that the OpAmp is ideal. If the gain V_o/V_{in} is

5

	<p>-12 determine the value of R in kΩ.</p>  <p style="text-align: center;">Fig. 5</p>	
	<p>b) Calculate the output voltage of an op-amp summing amplifier for the following sets of voltages and resistors. Use $R_f = 1\text{ M}$ in all cases.</p> <p>a. $V_1 = +1\text{ V}$, $V_2 = +2\text{ V}$, $V_3 = +3\text{ V}$, $R_1 = 500\text{ k}$, $R_2 = 1\text{ M}$, $R_3 = 1\text{ M}$.</p> <p>b. $V_1 = -2\text{ V}$, $V_2 = +3\text{ V}$, $V_3 = +1\text{ V}$, $R_1 = 200\text{ k}$, $R_2 = 500\text{ k}$, $R_3 = 1\text{ M}$</p>	5
	<p>c) Determine the output voltage of an op-amp for input voltages of $V_{i1} = 200\text{ mV}$ and $V_{i2} = 100\text{ mV}$. The amplifier has a differential gain of $A_d = 4000$ and the value of CMRR is:</p> <p>i. 150.</p> <p>ii. 10000 .</p>	6
	<p>d) What is precision rectifier ? Explain.</p>	4
4.	<p>a) Derive the output of log and antilog amplifier.</p>	10
	<p>b) Derive the expression for output voltage of an OpAmp in terms of A_d, V_d, V_c and CMRR.</p>	10
5.	<p>a) Draw and explain the circuits for amplifying the product and ratio of two voltages.</p>	10
	<p>b) Explain the working of monostable multivibrator using NE555 timer.</p>	10
6.	<p>Write short notes on any two of the following</p>	10x2=20
	<p>a) Schmitt Trigger</p>	
	<p>b) Phase Shift Oscillator</p>	
	<p>c) PLL</p>	
	<p>d) Instrumentation Amplifier</p>	