

2025

ANALOG INTEGRATED CIRCUITS

Full Marks : 100

Time : Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

1. a) Calculate the single-ended output voltage V_{o1} and Common mode gain for the circuit of Fig.1. 10

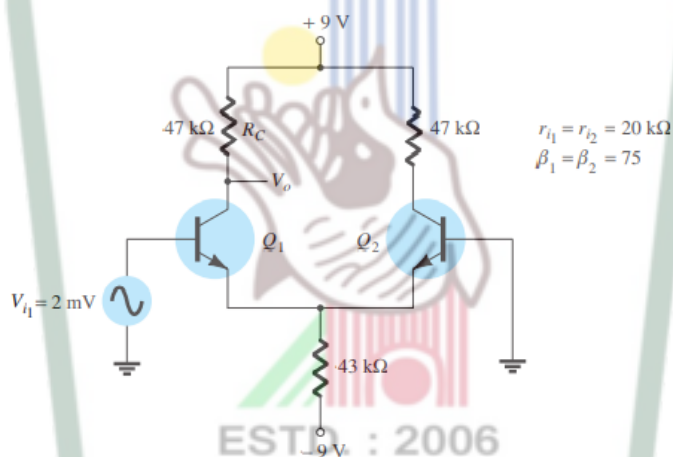


Fig.1

- b) Determine the output of an inverting amplifier and a non-inverting amplifier if $R_1=100\text{K}\Omega$, $R_f=500\text{K}\Omega$, and $V_i=2\text{V}$. 5
- c) Calculate the output voltage of an op-amp summing amplifier for the following sets of voltages and resistors. Use $R_f = 1\text{M}\Omega$ in all cases. 5
- i. $V_1 = +1\text{V}$, $V_2 = +2\text{V}$, $V_3 = +3\text{V}$, $R_1 = 500\text{K}\Omega$, $R_2 = 1\text{M}\Omega$, $R_3 = 1\text{M}\Omega$.
- ii. $V_1 = -2\text{V}$, $V_2 = +3\text{V}$, $V_3 = +1\text{V}$, $R_1 = 200\text{K}\Omega$, $R_2 = 500\text{K}\Omega$, $R_3 = 1\text{M}\Omega$.
2. a) Derive the output of Integrator and Differentiator using OpAmp. 10
- b) Determine the output voltage of the circuit of Fig. 3. 5

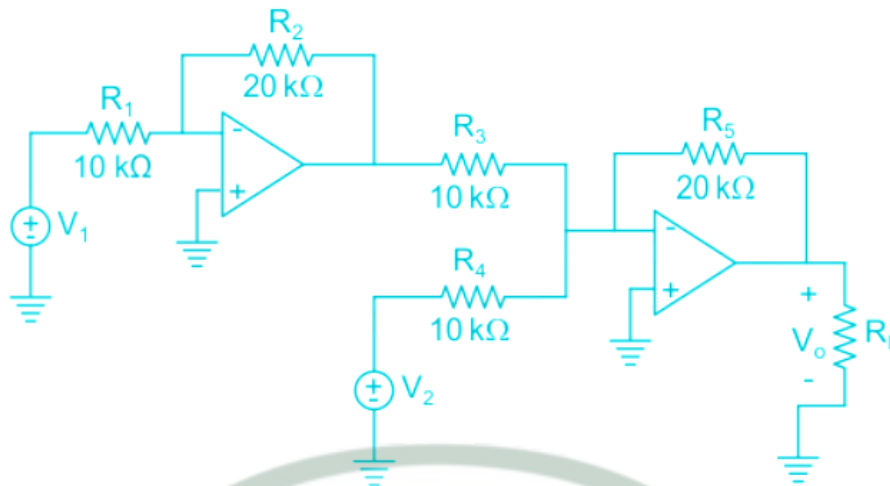


Fig. 3

- c) An ideal Op-Amp circuit shown below, $R_1=3k\Omega$, $R_2=1k\Omega$ and $V_i=0.5\sin\omega t$. Determine the potential at point P and amplitude of V_o . 5

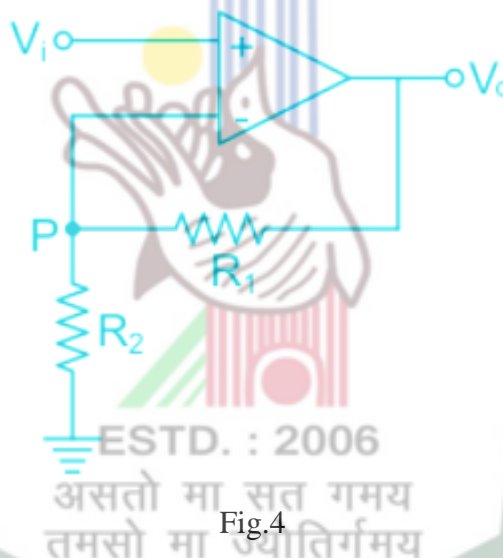


Fig.4

3. a) Derive the expression for Output offset voltage of an OpAmp due to Input offset Voltage and Input Offset Current. 10
- b) Draw and explain the circuits for amplifying the product of two voltages. 5
- c) Determine the output voltage of an op-amp for input voltages of $V_{i1} = 200$ mV and $V_{i2} = 100$ mV. The amplifier has a differential gain of $A_d = 4000$ and the value of CMRR is: 5
 - i. 150.
 - ii. 10000 .
4. a) Derive the output of log and antilog amplifier. 10
- b) Determine overall voltage gain of the circuit shown in fig. 5 5

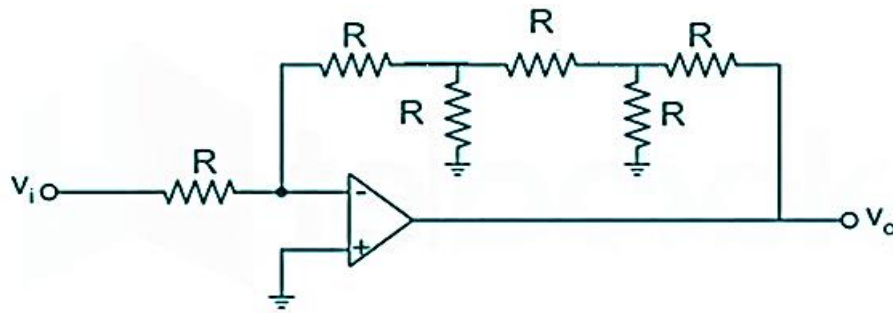


Fig.3

- c) What is Schmitt trigger? For the operational amplifier circuit shown, the output saturation voltages are $\pm 15V$. The upper and lower threshold voltages for the circuit are, respectively.

5

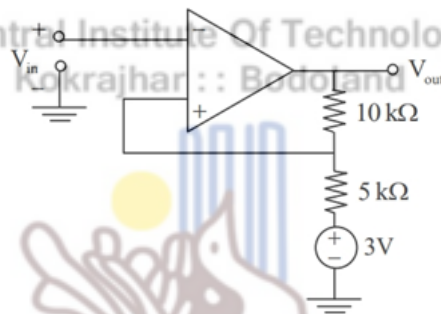


Fig. 6

5. a) What is a multivibrator? Explain an astable and a monostable multivibrator with OPamp. 10
- b) Explain the working of monostable multivibrator using NE555 timer. 10
6. Write short notes on any two of the following 10x2=20
 - a) Wein Bridge Oscillator
 - b) Phase Shift Oscillator
 - c) PLL