

2024

DIGITAL ELECTRONICS

Full Marks: 100


Time: Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

1. a) i) Hexadecimal Number that comes before A000 (H) and after A9FF (H) are- 10 x 2=20
- ii) Addition of 1's complement of an 8-bit number Y to another number (00001001), results in a 9-bit number (100000011). Find Y.
- iii) The output of a 4-input Ex-NOR gate is _____ when the number of inputs that are HIGH is even.
- iv) $(\quad)_7 = (25)_{10} = (\quad)_6$
- v) Minimum number of half adders required to add two 8-bit data is-
- vi) If the number of input lines in a Multiplexer is 36, then the minimum number of select lines required is _____.
- vii) In a five variable K-Map, a group having eight elements/squares will result in a term having _____ variables.
- viii) In a 3-bit asynchronous UP-counter with outputs Q₂, Q₁, Q₀, the output Q₂ is connected via a NOT gate to the Clear inputs of all the flip-flops. How many stable states will the counter have?
- ix) For an active HIGH edge triggered J-K flip-flop, the inputs J and K are permanently tied to logic '1'. What will be the output of the flip-flop in the third clock pulse if the present output is LOW?
- x) It is required to design a Counter capable of counting up to 2000 items. How many flip-flops will be required?

 2. a) Find the output expression for D and derive the truth table and minimize the expression if possible. 5



- b) Minimize the Boolean function- $(A \cdot B + A \cdot \bar{B})(\bar{A} + A \cdot B \cdot C + \bar{B} \cdot C)$ 2

- c) Implement Ex-OR and EX-NOR gates by using only NOR gates. 2+2 = 4

- d) Minimize using K-Map technique- 4+5 = 9

i) $F(A,B,C,D) = \sum m(0,1,4,5,7,8,12,13) + \sum d(3,10,15)$


ii) $F(A,B,C,D,E) = \sum m(1,6,7,8,9,15,16,19,29,30,31) + \sum d(0,1,5,20,28)$

3. a) Explain the working of a full-adder circuit with proper diagram and truth table. 5

- b) Explain the working of a 1-bit Magnitude Comparator circuit with the help of its truth table and logic diagram. 5

- c) Implement the Boolean function $Y(A,B,C) = \sum m(1,2,5,6)$ with a 4:1 MUX and few additional gates. 6

- d) Find out the expression for Y- 4

 


4. a) Implement a Full-subtractor with a 3-to-8-line Decoder and few additional gates. 5

- b) Construct an Active-LOW S-R latch with NAND gates and find out the characteristic equation of the output from its characteristic table. 5

- c) Differentiate between Level triggered flip-flops and Edge triggered flip-flops. 2

 - d) For an edge triggered J-K flip-flop with Preset and Clear inputs, find out the status of Q_{n+1} immediately after it is clocked for the following four conditions. (Assume $Q_n=0$) 4
- i) $J = 0, K = 0, Pr = 1, Cr = 1$
 - ii) $J = 1, K = 0, Pr = 1, Cr = 1$
 - iii) $J = 0, K = 0, Pr = 1, Cr = 0$
 - iv) $J = 0, K = 1, Pr = 0, Cr = 1$
- e) A 100 kHz clock signal is applied to a J-K flip-flop with $J = K = 1$. Determine the frequency of Q_{n+1} and find out the time required by the flip-flop to produce five number of HIGH outputs. 4
5. a) Implement a D-flip-flop using a J-K flip-flop. 6
- b) Design a modulo-5 asynchronous DOWN counter. 6
- c) Design a synchronous counter that has the following sequence- 8
000->010->101->110->100->111->000
6. a) Explain the working of a 4-bit storage Register. 6
- b) For the J-K flip-flop shown in the diagram below, find out the Characteristic Table and Transition Table in terms of the input variables A and B. 6



- c) Implement a 3-bit binary-to-gray converter circuit with the help of a suitable PLA. 8