


DIGITAL ELECTRONICS (UIE403)
End-Term Examination-2025
Full Marks- 100
Answer Question No.1 and any four from the rest

Q1: a) Answer the following questions-

10 X 2 = (20)

- i) $()_7 = (25)_{10} = ()_5$
- ii) Product-of-sum expression for AND gate is-
- iii) Addition of 2's complement of a binary number 'X' to a binary number $(1100)_2$ results in $(1000)_2$ with a carry. Find X.
- iv) For a Hex-to-seven-segment-display decoder, if the input in binary is $(1111)_2$, the output bits for (a,b,c,d,e,f,g) will be _____.
- v) If all the inputs of a 4:1 MUX are tied to logic '1', then the expression for the output Y is _____.
- vi) For a high priority octal-to-binary encoder, if the input stream is $(01100111)_2$, the output is _____.
- vii) If both the inputs of an edge triggered J-K flip-flop are permanently tied to logic '1', what will be its output state after the 4th clock pulse if the present output before the application of clock input is 1.
- viii) Modulus of a counter is defined as _____.
- ix) Number of address lines required for a 2048 X 8-bit memory chip is _____.
- x) If the present state of a J-K flip-flop is 1, then the inputs required at J&K to retain the output are ____.

 Q2: a) For the logic circuit given below, answer the following questions-




- i) Find out the expression and truth table for Y.
- ii) Identify the function achieved by the given circuit.
- iii) What needs to be done in the circuit to make the output expression $Y = A$?

2 + 2 = (4)

(2)

(2)

 b) For the logic circuit diagram given below, answer the following questions-



- i) Find out the expression and truth table for Y.
- ii) Minimize the output expression.

2 + 2 = (4)

(2)

c) Explain the working of a 4-bit binary adder with the help of proper functional block diagram.


(6)

Q3: a) Explain the working of an Active HIGH J-K flip-flop with Preset and Clear inputs. (5)

b) It is required to design a digital keypad with six switches named as S0, S1, S2, S3, S4, S5 that will produce the binary equivalent of the switch's numbers corresponding to a HIGH input from each of these switches. Determine the truth table and draw the logic circuit with basic gates. (5)


c) Design a MOD-5 asynchronous UP counter that resets itself after the last stable state. (6)

 d) Find out the characteristic table and the characteristic equation for the J-K flip-flop configured as below in terms of A and B inputs. (4)



Q4: a) Implement a T-flip flop with a J-K flip-flop. (4)

 b) Assuming the counter is reset initially and configured as below, answer the following questions-



- Is the counter shown above synchronous or asynchronous? (1)
- Draw the timing diagram of Q3, Q2, Q1 & Q0 for at least six clock pulses. (4)
- State whether the counter is an UP counter or a DOWN counter. (1)
- What is the modulus of the counter? (2)
- Write down the whole sequence of the counter with Q3 as MSB and Q0 as LSB. (3)
- If the clock frequency is 2 KHz, what will be the frequencies of Q3 and Q2? (2)
- What will be the modulus of the counter if Q1 replaces Q2 at the input of the NAND gate? (2)
- What can be done to reverse the sequence of the counter above? (1)


Q5: a) With a suitable PLA, implement a full-adder circuit. (6)

b) Design a counter that will have the following sequence- (6)

0-4-2-5-7-0

c) State two differences between a Combinational circuit and a Sequential circuit. (2)

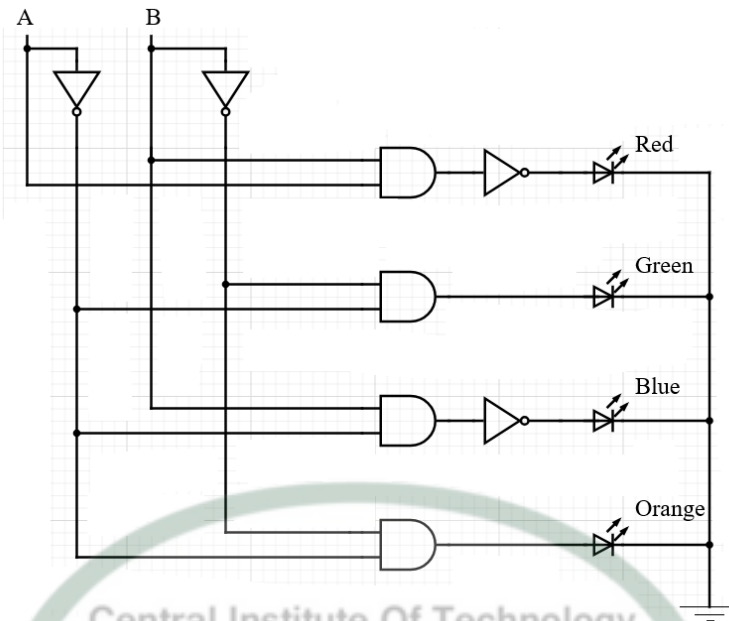d) For the diagram given below, answer the following questions-



- Which of the LEDs will be turned ON if $A = B = 0$? (2)
- What inputs should be applied at A & B to turn ON only the RED LED? (2)
- What inputs should be applied at A & B to turn ON only the BLUE LED? (2)

Q6: a) Implement the Boolean function $Y(A,B,C) = \sum m(0,2,5,6)$ with the help of a 4:1 MUX and few additional gates. (4)

b) Draw the logic circuit diagram of an Active-LOW S-R latch with NAND gates and state its characteristic table. Also, derive the excitation table of the latch from the characteristic table. $4 + 2 = (6)$

c) A memory chip is built with 256 registers with each register capable of storing 4 bits.

- What is the size of the memory chip in bytes? (1)
- How many address lines will be required to address these registers? (1)
- What will be the address of the first and the last registers in Hex? (2)
- How many such chips will be required to build a 1 Kbyte memory system? (2)

d) Consider a three-input Ex-OR gate where A and B are two of the inputs and the third input is permanently tied to logic '1'. Find out the truth table. (2)

e) Implement an Ex-NOR gate using NAND gates only. (2)

.....