

2025

ELECTRONIC INSTRUMENTATION


Full Marks: 100

Time: Three hours

The figures in the margin indicate full marks for the questions.

Answer any five questions.

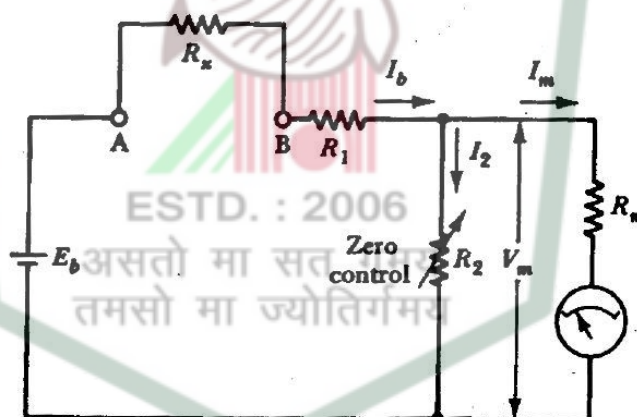1. a) What do you mean by loading effects of an instrument? Explain the operation of a transistor-based electronic DC voltmeter. (2+5=7)
- b) How can you measure a very small ac voltage using an OPAMP-based electronic voltmeter-explain with the help of circuit diagram (6)
- c) An ohmmeter circuit has $E_b=1.5$ V, $R_1=15k\Omega$, $R_m=50\Omega$, $R_2=50\Omega$ and meter FSD=50 μ A. Determine the ohmmeter scale reading at 0.5 FSD and the new resistance value of R_2 to compensate when the E drops to 1.3 V. (7)



2. a) Explain the operation of an electronic meter for the measurement of inductance? (5)
- b) Draw a circuit diagram for generating a triangular wave and explain its operation. (5)
- c) Explain how a PLL generates signals of desired frequency? (6)
- d) What are the different types of noises found in electronic systems? Write a few applications of Schmitt trigger circuit. (2+2=4)

- 3 a) Explain how a sweep frequency generator works? (6)
- b) What are the functions of a signal analyzer? Explain the working principle of spectrum analyzer. (1+6=7)
- c) With the help of schematic diagram explain how a cathode ray tube works? (7)
- 4 a) How does a sawtooth signal generator provide the time base in a CRO? Explain with the help of circuit diagram. (6)
- b) Which voltages are applied in the horizontal and vertical deflection plates? Draw the equivalent circuit diagram of 10:1 oscilloscope probe when connected to source and CRO. Also obtain the expression of output voltage at the CRO. (2+2+2=6)
- c) A 250 Hz triangular wave with a peak amplitude of 20 V is applied to the vertical deflecting plates of a CRT. A 500 Hz sawtooth wave with a peak amplitude of 40 V is applied to the horizontal deflecting plates. The CRT has a vertical deflection sensitivity of 0.2 cm/V and a horizontal deflection sensitivity of 0.1 cm/V. Determine the waveform displayed on the screen. (8)
- 5 a) Explain how a sampling oscilloscope works? (5)
- b) What is a Lissajous pattern or curve? Draw the Lissajous pattern for two signals with the frequency ratio of 2:1 in themselves. (1+2=3)
- c) What qualities are desired in a CRO in terms of input impedance, frequency and display time? What are the differences between a CRO and a DSO? How is the analog voltage stored digitally in the DSO? Explain the working principle of a DSO. (2+2+8=12)
- 6 a) What is a quantization error? What will be the quantization error for a 2 bit ADC? What are the different types of ADC? Explain the working principle of a ramp type digital voltmeter (DVM) with the help of block diagram. (1+2+2+6=11)
- b) What are the advantages of digital instruments over analog instruments? With the help of block diagram explain how a digital frequency meter work? (2+7=9)
- 7 a) Give a brief illustration about dot matrix and 7 segment display. (2+2+6=10)
Explain the operation of a pen type strip chart recorder. (10)
- b) Write short notes on any two of the following (2 x 5=10)
- X-Y recorder
 - IEEE 488 bus
 - Magnetic tape recorder
 - Interference and screening